

CALCULATE THE ERROR IN THE AMMETER WHICH READS 3.25 A IN A CIRCUIT HAVING A SERIES STANDARD RESISTANCE

CALCULATE THE ERROR IN THE AMMETER WHICH READS 3.25 A IN A CIRCUIT HAVING A SERIES STANDARD RESISTANCE

INTRODUCTION

IN ELECTRICAL MEASUREMENTS, PRECISION AND ACCURACY ARE PARAMOUNT. INSTRUMENTS LIKE AMMETERS ARE USED TO MEASURE CURRENT FLOW IN VARIOUS CIRCUITS, BUT THEIR READINGS CAN SOMETIMES BE AFFECTED BY INTERNAL AND EXTERNAL FACTORS. ONE COMMON SCENARIO INVOLVES AN AMMETER READING A CURRENT OF 3.25 A WHEN CONNECTED IN A CIRCUIT THAT INCLUDES A KNOWN SERIES RESISTANCE. UNDERSTANDING HOW TO ACCURATELY CALCULATE THE MEASUREMENT ERROR UNDER THESE CONDITIONS IS ESSENTIAL FOR ENSURING THE RELIABILITY OF ELECTRICAL MEASUREMENTS, WHETHER IN LABORATORY TESTING, MAINTENANCE, OR INDUSTRIAL APPLICATIONS.

IN THIS ARTICLE, WE EXPLORE HOW TO CALCULATE THE ERROR IN AN AMMETER READING OF 3.25 A WHEN THE INSTRUMENT IS CONNECTED IN A CIRCUIT WITH A SERIES STANDARD RESISTANCE. WE WILL DELVE INTO THE UNDERLYING PRINCIPLES, NECESSARY FORMULAS, AND STEP-BY-STEP PROCEDURES TO DETERMINE THE ERROR, CONSIDERING FACTORS SUCH AS INTERNAL RESISTANCE OF THE AMMETER AND THE EFFECT OF THE SERIES RESISTANCE ON THE MEASUREMENT.

BASICS OF AMMETER MEASUREMENT AND ERROR

WHAT IS AN AMMETER?

AN AMMETER IS AN ELECTRICAL INSTRUMENT USED TO MEASURE CURRENT FLOWING THROUGH A CIRCUIT. IT IS CONNECTED IN SERIES WITH THE CIRCUIT ELEMENTS TO ALLOW THE CURRENT TO PASS THROUGH IT FOR MEASUREMENT. TO ENSURE ACCURATE READINGS, THE AMMETER SHOULD HAVE A VERY LOW INTERNAL RESISTANCE, MINIMIZING ITS IMPACT ON THE CIRCUIT.

SOURCES OF ERROR IN AMMETER READINGS

ERRORS IN AMMETER READINGS CAN ARISE FROM MULTIPLE SOURCES, INCLUDING:

- INTERNAL RESISTANCE OF THE AMMETER: EVEN THE BEST AMMETERS HAVE A FINITE INTERNAL RESISTANCE, WHICH CAN AFFECT THE CURRENT FLOW.
- SERIES RESISTANCE IN THE CIRCUIT: ADDITIONAL RESISTANCE IN SERIES WITH THE AMMETER INFLUENCES THE CURRENT MEASURED.
- CALIBRATION ERRORS: DEVIATIONS FROM THE TRUE CALIBRATION CAN LEAD TO INACCURATE READINGS.
- TEMPERATURE EFFECTS: CHANGES IN TEMPERATURE CAN AFFECT THE RESISTANCE OF CIRCUIT ELEMENTS AND THE AMMETER.
- PARASITIC RESISTANCES AND EXTERNAL FACTORS: LEAD RESISTANCE, CONTACT RESISTANCE, AND ELECTROMAGNETIC INTERFERENCE.

IN OUR SPECIFIC CASE, THE FOCUS IS ON THE EFFECT OF A KNOWN SERIES RESISTANCE AND HOW IT INFLUENCES THE MEASUREMENT OF CURRENT, LEADING TO POTENTIAL MEASUREMENT ERROR.

UNDERSTANDING SERIES RESISTANCE AND ITS IMPACT

SERIES RESISTANCE IN A CIRCUIT

WHEN A RESISTOR (KNOWN AS THE SERIES STANDARD RESISTANCE) IS CONNECTED IN SERIES WITH AN AMMETER, THE TOTAL RESISTANCE IN THE CIRCUIT INCREASES. THE CURRENT FLOWING THROUGH THE CIRCUIT IS THEN DETERMINED BY THE TOTAL RESISTANCE, WHICH AFFECTS THE MEASUREMENT.

IF WE DENOTE:

- R_s = SERIES STANDARD RESISTANCE
- R_i = INTERNAL RESISTANCE OF THE AMMETER
- V = VOLTAGE APPLIED ACROSS THE CIRCUIT
- I_{ACTUAL} = ACTUAL CURRENT FLOWING THROUGH THE CIRCUIT

THE TOTAL RESISTANCE IN THE CIRCUIT BECOMES:

$$[R_{\text{TOTAL}} = R_s + R_i]$$

THE CURRENT MEASURED BY THE AMMETER, WHICH IS DESIGNED TO MEASURE THE CURRENT THROUGH THE CIRCUIT, WILL BE:

$$[I_{\text{MEASURED}} = \frac{V}{R_s + R_i}]$$

HOWEVER, THE ACTUAL CURRENT IN THE CIRCUIT WITHOUT THE SERIES RESISTANCE (OR WITH THE ACTUAL RESISTANCE IN THE CIRCUIT) MAY DIFFER, LEADING TO MEASUREMENT ERRORS.

EFFECT OF SERIES RESISTANCE ON MEASUREMENT ACCURACY

THE PRESENCE OF SERIES RESISTANCE REDUCES THE CURRENT FLOWING THROUGH THE CIRCUIT, WHICH THE AMMETER READS AS THE CURRENT VALUE. IF THE INTERNAL RESISTANCE OF THE AMMETER IS NOT NEGLIGIBLE, THE READING MAY DEVIATE FROM THE TRUE CURRENT. CALCULATING THIS DEVIATION ENABLES US TO UNDERSTAND THE MEASUREMENT ERROR.

CALCULATING THE ERROR IN AMMETER READING

STEP 1: DEFINE KNOWN AND UNKNOWN QUANTITIES

TO PROCEED, WE NEED TO IDENTIFY ALL KNOWN QUANTITIES AND THE ASSUMPTIONS:

- THE AMMETER READS 3.25 A IN THE CIRCUIT.
- THE SERIES STANDARD RESISTANCE R_s IS KNOWN (FROM CIRCUIT SPECIFICATIONS).
- THE INTERNAL RESISTANCE OF THE AMMETER R_i IS KNOWN OR CAN BE ESTIMATED.
- THE VOLTAGE V ACROSS THE CIRCUIT IS EITHER KNOWN OR CAN BE CALCULATED.

IN MANY PRACTICAL SCENARIOS, THE GOAL IS TO FIND THE TRUE CURRENT I_{TRUE} IN THE CIRCUIT BASED ON THE MEASURED CURRENT I_{MEASURED} AND THE KNOWN RESISTANCES.

STEP 2: ESTABLISH THE RELATIONSHIP BETWEEN MEASURED AND TRUE CURRENTS

ASSUMING THE AMMETER IS IDEAL EXCEPT FOR ITS INTERNAL RESISTANCE, THE MEASURED CURRENT I_{MEASURED} IS AFFECTED BY THE INTERNAL RESISTANCE:

$$[I_{\text{MEASURED}} = \frac{V}{R_s + R_i}]$$

BUT SINCE V IS THE SAME IN BOTH CASES, AND THE TRUE CURRENT I_{TRUE} IN THE CIRCUIT WITHOUT THE ADDITIONAL SERIES RESISTANCE IS:

$$I_{\text{TRUE}} = \frac{V}{R_{\text{LOAD}}}$$

WHERE R_{LOAD} IS THE LOAD RESISTANCE IN THE CIRCUIT.

IF THE SERIES RESISTANCE R_S IS ADDED, THE CURRENT REDUCES TO:

$$I_{\text{MEASURED}} = \frac{V}{R_S + R_{\text{LOAD}} + R_I}$$

REARRANGING FOR V :

$$V = I_{\text{MEASURED}} (R_S + R_{\text{LOAD}} + R_I)$$

SIMILARLY, THE TRUE CURRENT I_{TRUE} (WITHOUT SERIES RESISTANCE):

$$I_{\text{TRUE}} = \frac{V}{R_{\text{LOAD}} + R_I}$$

SUBSTITUTING V :

$$I_{\text{TRUE}} = \frac{I_{\text{MEASURED}} (R_S + R_{\text{LOAD}} + R_I)}{R_{\text{LOAD}} + R_I}$$

THIS EQUATION ENABLES CALCULATION OF THE TRUE CURRENT BASED ON THE MEASURED CURRENT AND KNOWN RESISTANCES.

STEP 3: CALCULATE THE ERROR

THE MEASUREMENT ERROR E CAN BE EXPRESSED AS:

$$E = \frac{I_{\text{TRUE}} - I_{\text{MEASURED}}}{I_{\text{TRUE}}} \times 100\%$$

ALTERNATIVELY, THE ABSOLUTE ERROR:

$$\Delta I = I_{\text{TRUE}} - I_{\text{MEASURED}}$$

USING THE EARLIER DERIVED RELATION, THE ERROR DEPENDS ON THE KNOWN RESISTANCES AND MEASURED CURRENT.

PRACTICAL EXAMPLE AND STEP-BY-STEP CALCULATION

SUPPOSE:

- R_S (SERIES RESISTANCE) = 10Ω
- R_I (INTERNAL RESISTANCE OF THE AMMETER) = 0.1Ω
- THE LOAD RESISTANCE R_{LOAD} IS UNKNOWN, BUT FOR THE PURPOSE OF CALCULATION, LET'S ASSUME $R_{\text{LOAD}} = 100 \Omega$
- THE AMMETER READS 3.25 A

STEP 1: CALCULATE THE VOLTAGE V ACROSS THE CIRCUIT:

$$\begin{aligned} V &= I_{\text{MEASURED}} (R_S + R_{\text{LOAD}} + R_I) \\ V &= 3.25 (10 + 100 + 0.1) \\ V &= 3.25 \times 110.1 \\ V &\approx 358.83 \text{ VOLTS} \end{aligned}$$

STEP 2: CALCULATE THE TRUE CURRENT I_{TRUE} WITHOUT THE SERIES RESISTANCE:

$$I_{\text{TRUE}} = \frac{V}{R_{\text{LOAD}} + R_i}$$

$$I_{\text{TRUE}} = \frac{358.83}{100 + 0.1}$$

$$I_{\text{TRUE}} \approx \frac{358.83}{100.1}$$

$$I_{\text{TRUE}} \approx 3.585 \text{ A}$$

STEP 3: DETERMINE THE ERROR:

$$\Delta I = I_{\text{TRUE}} - I_{\text{MEASURED}} = 3.585 - 3.25 = 0.335 \text{ A}$$

STEP 4: CALCULATE PERCENTAGE ERROR:

$$\text{Error} = \frac{0.335}{3.585} \times 100\% \approx 9.34\%$$

THIS INDICATES THAT THE AMMETER'S READING UNDER THESE CONDITIONS IS APPROXIMATELY 9.34% LOWER THAN THE ACTUAL CURRENT DUE TO THE SERIES RESISTANCE AND INTERNAL RESISTANCE EFFECTS.

FACTORS AFFECTING THE ACCURACY AND MINIMIZING ERROR

1. USE OF LOW-RESISTANCE AMMETERS

CHOOSING AMMETERS WITH MINIMAL INTERNAL RESISTANCE REDUCES MEASUREMENT DEVIATION. MICROAMMETERS AND DIGITAL MULTIMETERS DESIGNED FOR LOW-RESISTANCE MEASUREMENTS ARE PREFERABLE.

2. PROPER CIRCUIT CONFIGURATION

ENSURING THAT THE AMMETER IS CORRECTLY CONNECTED IN SERIES AND THAT ADDITIONAL RESISTANCES ARE MINIMIZED OR ACCOUNTED FOR IMPROVES ACCURACY.

3. CALIBRATION AND COMPENSATION

REGULAR CALIBRATION OF THE AMMETER AND APPLYING CORRECTION FACTORS BASED ON KNOWN INTERNAL RESISTANCE CAN HELP COMPENSATE FOR MEASUREMENT ERRORS.

4. ACCURATE KNOWLEDGE OF CIRCUIT RESISTANCES

PRECISELY KNOWING THE SERIES RESISTANCE AND LOAD RESISTANCE ALLOWS FOR MORE ACCURATE ERROR CALCULATIONS AND CORRECTIONS.

CONCLUSION

CALCULATING THE ERROR IN AN AMMETER READING, ESPECIALLY WHEN CONNECTED WITH A SERIES STANDARD RESISTANCE, INVOLVES UNDERSTANDING THE INTERPLAY BETWEEN THE CIRCUIT'S RESISTANCES, THE AMMETER'S INTERNAL RESISTANCE, AND THE APPLIED VOLTAGE. BY ESTABLISHING THE RELATIONSHIPS AMONG THESE QUANTITIES, ONE CAN DETERMINE THE TRUE CURRENT AND QUANTIFY THE MEASUREMENT ERROR.

IN PRACTICAL APPLICATIONS, MINIMIZING MEASUREMENT ERROR REQUIRES SELECTING APPROPRIATE INSTRUMENTS, ENSURING

PROPER CIRCUIT CONFIGURATION, AND APPLYING CORRECTION FACTORS WHEN NECESSARY. MASTERY OF THESE PRINCIPLES IS ESSENTIAL FOR ELECTRICAL ENGINEERS, TECHNICIANS, AND STUDENTS AIMING FOR PRECISE CURRENT MEASUREMENTS IN VARIOUS ELECTRICAL AND ELECTRONIC SYSTEMS.

ALWAYS REMEMBER THAT THE ACCURACY OF YOUR MEASUREMENTS DEPENDS NOT ONLY ON THE INSTRUMENT'S QUALITY BUT ALSO ON UNDERSTANDING AND ACCOUNTING FOR THE VARIOUS

FREQUENTLY ASKED QUESTIONS

HOW DO YOU CALCULATE THE ERROR IN AN AMMETER READING OF 3.25 A WITH A SERIES STANDARD RESISTANCE?

TO CALCULATE THE ERROR, DETERMINE THE EXPECTED CURRENT WITHOUT THE SERIES RESISTANCE, COMPARE IT WITH THE ACTUAL READING, AND THEN FIND THE DIFFERENCE. ALTERNATIVELY, USE THE KNOWN RESISTANCE VALUE AND THE VOLTAGE TO FIND THE ACTUAL CURRENT AND COMPARE IT WITH THE AMMETER READING.

WHAT IS THE FORMULA FOR CALCULATING THE ERROR IN AN AMMETER WHEN A SERIES RESISTANCE IS ADDED?

$\text{Error} = (I_{\text{ACTUAL}} - I_{\text{AMMETER}}) / I_{\text{ACTUAL}} \times 100\%$, WHERE I_{ACTUAL} IS THE TRUE CURRENT CALCULATED USING OHM'S LAW WITH THE SERIES RESISTANCE, AND I_{AMMETER} IS THE READING SHOWN BY THE AMMETER.

HOW DOES ADDING A SERIES RESISTANCE AFFECT THE ACCURACY OF AN AMMETER READING?

ADDING A SERIES RESISTANCE CAUSES A VOLTAGE DIVISION, WHICH CAN REDUCE THE CURRENT PASSING THROUGH THE AMMETER, LEADING TO AN INACCURATE READING IF NOT PROPERLY COMPENSATED. THE ERROR DEPENDS ON THE RESISTANCE VALUE AND THE CIRCUIT VOLTAGE.

WHAT STEPS ARE INVOLVED IN CALCULATING THE ERROR IN THE AMMETER READING OF 3.25 A WITH A KNOWN SERIES RESISTANCE?

FIRST, DETERMINE THE CIRCUIT VOLTAGE OR THE ACTUAL CURRENT USING OHM'S LAW CONSIDERING THE SERIES RESISTANCE. THEN, COMPARE THIS TRUE CURRENT WITH THE AMMETER READING TO FIND THE ERROR PERCENTAGE.

IF AN AMMETER READS 3.25 A WITH A SERIES RESISTOR OF 10 OHMS IN THE CIRCUIT, HOW DO YOU FIND THE ACTUAL CURRENT?

ASSUMING THE SUPPLY VOLTAGE IS KNOWN, USE OHM'S LAW: $I_{\text{ACTUAL}} = V / (R_{\text{TOTAL}})$, WHERE R_{TOTAL} INCLUDES THE SERIES RESISTANCE. IF THE SUPPLY VOLTAGE ISN'T GIVEN, THE ERROR CALCULATION CANNOT BE COMPLETED ACCURATELY.

WHY IS IT IMPORTANT TO ACCOUNT FOR SERIES RESISTANCE WHEN MEASURING CURRENT WITH AN AMMETER?

BECAUSE SERIES RESISTANCE CAN CAUSE VOLTAGE DROPS THAT ALTER THE ACTUAL CURRENT IN THE CIRCUIT, LEADING TO INACCURACIES IN THE AMMETER READING IF NOT PROPERLY CONSIDERED.

CAN THE ERROR IN THE AMMETER READING BE MINIMIZED BY REMOVING THE SERIES

RESISTANCE?

YES, REMOVING OR REDUCING THE SERIES RESISTANCE MINIMIZES THE VOLTAGE DROP ACROSS IT, RESULTING IN A MORE ACCURATE CURRENT MEASUREMENT BY THE AMMETER.

WHAT ROLE DOES THE INTERNAL RESISTANCE OF THE AMMETER PLAY IN CALCULATING MEASUREMENT ERROR?

THE INTERNAL RESISTANCE OF THE AMMETER ADDS TO THE SERIES RESISTANCE, AFFECTING THE TOTAL CIRCUIT RESISTANCE AND POTENTIALLY CAUSING MEASUREMENT ERRORS, ESPECIALLY IN LOW-CURRENT CIRCUITS.

HOW DOES THE ACCURACY OF THE AMMETER INFLUENCE THE CALCULATION OF ERROR IN THE PRESENCE OF SERIES RESISTANCE?

A MORE ACCURATE AMMETER REDUCES MEASUREMENT UNCERTAINTIES, MAKING THE CALCULATED ERROR MORE RELIABLE. CONVERSELY, AN IMPRECISE AMMETER CAN INTRODUCE ADDITIONAL ERROR, COMPLICATING THE CALCULATION.

WHAT INFORMATION IS NECESSARY TO ACCURATELY CALCULATE THE ERROR IN AN AMMETER READING WHEN A SERIES RESISTANCE IS PRESENT?

THE KNOWN CIRCUIT VOLTAGE, THE VALUE OF THE SERIES RESISTANCE, AND THE AMMETER READING ARE NECESSARY. WITH THESE, YOU CAN COMPUTE THE TRUE CURRENT AND DETERMINE THE PERCENTAGE ERROR.

ADDITIONAL RESOURCES

AMMETER ERROR CALCULATION: AN EXPERT GUIDE TO IN-CIRCUIT MEASUREMENT WITH SERIES STANDARD RESISTANCE

INTRODUCTION

IN THE REALM OF ELECTRICAL MEASUREMENTS, PRECISION AND ACCURACY ARE PARAMOUNT. WHEN IT COMES TO AMMETERS—FUNDAMENTAL TOOLS USED TO MEASURE CURRENT—UNDERSTANDING AND CALCULATING POTENTIAL ERRORS IS CRUCIAL FOR ENSURING RELIABLE DATA. THIS ARTICLE DELVES DEEP INTO THE PROCESS OF CALCULATING THE ERROR IN AN AMMETER THAT READS 3.25 A WHILE CONNECTED IN CIRCUIT WITH A SERIES STANDARD RESISTANCE. WHETHER YOU'RE AN ELECTRICAL ENGINEER, TECHNICIAN, OR STUDENT, MASTERING THIS CALCULATION ENHANCES YOUR ABILITY TO INTERPRET MEASUREMENTS ACCURATELY AND TROUBLESHOOT EFFECTIVELY.

UNDERSTANDING THE CONTEXT

BEFORE WE PROCEED WITH THE ERROR CALCULATION, IT'S ESSENTIAL TO COMPREHEND THE FUNDAMENTAL CONCEPTS INVOLVED:

- AMMETER: A DEVICE DESIGNED TO MEASURE CURRENT FLOWING THROUGH A CIRCUIT, TYPICALLY CONNECTED IN SERIES.
- IN-CIRCUIT MEASUREMENT: THE PROCESS OF MEASURING CURRENT WHILE THE MEASURING INSTRUMENT IS PART OF THE CIRCUIT, WHICH CAN INTRODUCE ERRORS.
- SERIES STANDARD RESISTANCE: A KNOWN, CALIBRATED RESISTANCE PLACED IN SERIES WITH THE AMMETER TO FACILITATE CERTAIN MEASUREMENT TECHNIQUES AND ERROR ANALYSIS.
- MEASUREMENT READING: THE VALUE DISPLAYED BY THE AMMETER; IN THIS CASE, 3.25 A.

WHY ERROR CALCULATION MATTERS

ERRORS IN MEASUREMENT CAN STEM FROM VARIOUS SOURCES, INCLUDING INSTRUMENT LIMITATIONS, CIRCUIT CONDITIONS, AND EXTERNAL FACTORS. QUANTIFYING THESE ERRORS ALLOWS FOR:

- IMPROVED ACCURACY: ADJUSTING READINGS OR CALIBRATION TO MINIMIZE ERRORS.
- RELIABILITY: ENSURING MEASUREMENTS ARE WITHIN ACCEPTABLE TOLERANCES FOR CRITICAL APPLICATIONS.
- TROUBLESHOOTING: IDENTIFYING POTENTIAL ISSUES IN THE MEASUREMENT SETUP OR CIRCUIT COMPONENTS.

TYPES OF ERRORS IN AMMETER MEASUREMENTS

UNDERSTANDING THE POTENTIAL ERRORS INVOLVED IS FUNDAMENTAL:

1. INSTRUMENTAL ERROR: DUE TO LIMITATIONS IN THE AMMETER'S DESIGN, CALIBRATION, OR INHERENT INACCURACIES.
2. LOADING ERROR: WHEN THE AMMETER'S INTERNAL RESISTANCE AFFECTS THE CIRCUIT, ALTERING THE CURRENT FLOW.
3. CONNECTION ERROR: POOR CONTACTS OR INCORRECT SETUP CAN INTRODUCE ADDITIONAL RESISTANCE.
4. EXTERNAL FACTORS: TEMPERATURE, ELECTROMAGNETIC INTERFERENCE, AND CIRCUIT CONDITIONS.

IN THIS ARTICLE, OUR FOCUS IS PRIMARILY ON LOADING ERRORS CAUSED BY THE SERIES STANDARD RESISTANCE, ALONG WITH THE INHERENT INSTRUMENTAL ERROR.

THE ROLE OF SERIES STANDARD RESISTANCE IN MEASUREMENT

IN MANY MEASUREMENT SETUPS, A KNOWN RESISTOR (STANDARD RESISTOR) IS PLACED IN SERIES WITH THE AMMETER. THIS CONFIGURATION SERVES MULTIPLE PURPOSES:

- CALIBRATION: TO VERIFY THE ACCURACY OF THE AMMETER.
- ERROR ANALYSIS: TO UNDERSTAND HOW ADDITIONAL RESISTANCE AFFECTS THE READING.
- CURRENT LIMITING: TO PREVENT EXCESSIVE CURRENT THAT COULD DAMAGE THE METER.

WHEN CONNECTED IN SERIES, THE TOTAL CIRCUIT RESISTANCE BECOMES THE SUM OF THE AMMETER'S INTERNAL RESISTANCE, THE SERIES STANDARD RESISTANCE, AND ANY OTHER CIRCUIT RESISTANCES.

THEORETICAL BACKGROUND FOR ERROR CALCULATION

TO ACCURATELY DETERMINE THE ERROR, WE NEED TO UNDERSTAND THE RELATIONSHIP BETWEEN THE MEASURED CURRENT, THE ACTUAL CURRENT, AND THE RESISTANCES INVOLVED.

SUPPOSE:

- (R_s) = SERIES STANDARD RESISTANCE
- (R_m) = INTERNAL RESISTANCE OF THE AMMETER
- (I_m) = MEASURED CURRENT (3.25 A)
- (I_{ACTUAL}) = ACTUAL CURRENT FLOWING IN THE CIRCUIT

THE FUNDAMENTAL PRINCIPLE IS:

$$V = I \times R_{\text{TOTAL}}$$

WHERE:

$$R_{\text{TOTAL}} = R_s + R_m + R_{\text{CIRCUIT}}$$

\]

IN MANY CASES, (R_{CIRCUIT}) IS EITHER KNOWN OR NEGLIGIBLE FOR THE CALCULATION.

STEP-BY-STEP ERROR CALCULATION

STEP 1: DETERMINE THE KNOWN PARAMETERS

- THE READ CURRENT: $(I_M = 3.25 \text{ A})$
- THE SERIES RESISTANCE: (R_S) (KNOWN VALUE)
- THE AMMETER'S INTERNAL RESISTANCE: (R_M) (PROVIDED BY THE MANUFACTURER)
- THE NOMINAL CIRCUIT CURRENT: (I_{TRUE}) (UNKNOWN, TO BE ESTIMATED)

STEP 2: ESTABLISH THE CIRCUIT CONDITIONS

ASSUMING THE MEASUREMENT SETUP INVOLVES A KNOWN VOLTAGE SOURCE (V) , THE ACTUAL CURRENT WITHOUT MEASUREMENT ERRORS IS:

$$I_{\text{ACTUAL}} = \frac{V}{R_S + R_M + R_{\text{CIRCUIT}}}$$

BUT SINCE THE ACTUAL VOLTAGE SOURCE IS OFTEN UNKNOWN, WE USE THE MEASURED CURRENT AND RESISTANCES TO ESTIMATE THE ERROR.

STEP 3: USE THE MEASUREMENT FORMULA

THE AMMETER READING IS BASED ON THE VOLTAGE ACROSS IT:

$$V_{\text{MEASURED}} = I_M \times R_M$$

HOWEVER, BECAUSE THE METER IS IN CIRCUIT WITH THE SERIES RESISTANCE, THE TOTAL VOLTAGE IS:

$$V_{\text{TOTAL}} = I_M \times (R_S + R_M + R_{\text{CIRCUIT}})$$

ASSUMING (R_{CIRCUIT}) IS NEGLIGIBLE OR KNOWN, THE ACTUAL CURRENT CAN BE APPROXIMATED AS:

$$I_{\text{ACTUAL}} = \frac{V_{\text{TOTAL}}}{R_S + R_M + R_{\text{CIRCUIT}}}$$

GIVEN THAT (V_{TOTAL}) IS UNKNOWN, BUT THE MEASUREMENT IS BASED ON THE VOLTAGE ACROSS THE METER, THE RELATIVE ERROR CAN BE DEDUCED.

STEP 4: CALCULATE THE ERROR

THE PERCENTAGE ERROR IN THE AMMETER READING:

$$\text{Error (\%)} = \frac{I_{\text{ACTUAL}} - I_M}{I_M} \times 100$$

OR, MORE PRACTICALLY, IF THE INTERNAL RESISTANCE (R_M) AND THE SERIES RESISTANCE (R_S) ARE KNOWN, THE

ACTUAL CURRENT CAN BE ESTIMATED AS:

$$I_{\text{ACTUAL}} \approx \frac{V}{R_s + R_m}$$

BUT SINCE (V) IS NOT DIRECTLY KNOWN, IT'S COMMON TO RELATE THE ERRORS BASED ON RESISTANCE RATIOS.

PRACTICAL CALCULATION WITH EXAMPLE VALUES

LET'S CONSIDER AN EXAMPLE WHERE:

- SERIES STANDARD RESISTANCE, $(R_s = 0.5\, \Omega)$
- AMMETER INTERNAL RESISTANCE, $(R_m = 0.1\, \Omega)$
- THE MEASURED CURRENT, $(I_m = 3.25\, A)$

STEP 1: CALCULATE THE VOLTAGE ACROSS THE AMMETER:

$$V_m = I_m \times R_m = 3.25\, A \times 0.1\, \Omega = 0.325\, V$$

STEP 2: ASSUME THE CIRCUIT VOLTAGE IS SUCH THAT:

$$V_{\text{TOTAL}} = I_{\text{TRUE}} \times (R_s + R_m)$$

IF THE AMMETER'S READING IS ACCURATE, THEN:

$$I_{\text{TRUE}} \approx \frac{V_{\text{TOTAL}}}{R_s + R_m}$$

BUT SINCE THE ACTUAL CIRCUIT VOLTAGE ISN'T GIVEN, WE CAN ESTIMATE THE ERROR IN THE READING BASED ON THE INFLUENCE OF THE SERIES RESISTANCE.

STEP 3: CALCULATING THE ERROR:

THE ACTUAL CURRENT (EXCLUDING THE EFFECT OF THE SERIES RESISTANCE) WOULD BE:

$$I_{\text{ACTUAL}} = \frac{V_{\text{TOTAL}}}{R_{\text{CIRCUIT}}}$$

BUT WITHOUT (V_{TOTAL}) , WE ANALYZE THE LOADING EFFECT OF THE SERIES RESISTOR.

THE ERROR IN THE AMMETER READING DUE TO SERIES RESISTANCE IS:

$$\text{ERROR} \approx \frac{R_s}{R_{\text{TOTAL}}} \times 100\%$$

WHERE:

$$R_{\text{TOTAL}} = R_s + R_m + R_{\text{CIRCUIT}}$$

\]

ASSUMING (R_{CIRCUIT}) IS NEGLIGIBLE OR KNOWN, THE ERROR PERCENTAGE BECOMES:

$$\text{Error} \approx \frac{R_s}{R_s + R_m} \times 100\%$$

PLUGGING IN THE VALUES:

$$\text{Error} \approx \frac{0.5}{0.5 + 0.1} \times 100\% = \frac{0.5}{0.6} \times 100\% \approx 83.33\%$$

THIS HIGH PERCENTAGE INDICATES THAT THE SERIES RESISTANCE SIGNIFICANTLY INFLUENCES THE MEASUREMENT, INTRODUCING A SIZEABLE ERROR.

NOTE: THIS SIMPLIFIED MODEL DEMONSTRATES THE IMPORTANCE OF SELECTING APPROPRIATE SERIES RESISTANCE AND UNDERSTANDING ITS IMPACT.

FACTORS AFFECTING ERROR MAGNITUDE

THE CALCULATED ERROR DEPENDS ON SEVERAL FACTORS:

- VALUE OF SERIES RESISTANCE (R_s): LARGER RESISTANCE INCREASES THE LOADING EFFECT, CAUSING HIGHER ERROR.
- INTERNAL RESISTANCE OF THE AMMETER (R_m): HIGHER INTERNAL RESISTANCE AMPLIFIES THE MEASUREMENT DEVIATION.
- CIRCUIT CONDITIONS: ACTUAL CIRCUIT RESISTANCE AND VOLTAGE INFLUENCE THE TRUE CURRENT.
- CALIBRATION AND INSTRUMENT QUALITY: WELL-CALIBRATED INSTRUMENTS REDUCE INSTRUMENTAL ERRORS.

STRATEGIES TO MINIMIZE MEASUREMENT ERROR

TO ENSURE ACCURATE READINGS, CONSIDER THE FOLLOWING:

- USE LOW-RESISTANCE SERIES RESISTORS: KEEP R_s MINIMAL TO REDUCE LOADING ERRORS.
- SELECT HIGH-QUALITY AMMETERS: INSTRUMENTS WITH LOW R_m AND HIGH PRECISION.
- CALIBRATE REGULARLY: ENSURE DEVICES ARE WITHIN CALIBRATION STANDARDS.
- PERFORM OPEN-CIRCUIT MEASUREMENTS: WHEN POSSIBLE, MEASURE CURRENT WITHOUT THE SERIES RESISTOR OR WITH KNOWN VALUES.
- APPLY CORRECTION FACTORS: ADJUST READINGS BASED ON CALCULATED OR KNOWN ERRORS.

FINAL REMARKS

CALCULATING THE ERROR IN AN AMMETER READING—PARTICULARLY WHEN IN-CIRCUIT MEASUREMENTS INVOLVE A SERIES STANDARD RESISTANCE—REQUIRES A THOROUGH UNDERSTANDING OF CIRCUIT THEORY, INSTRUMENT SPECIFICATIONS, AND MEASUREMENT PRINCIPLES. WHILE SIMPLIFIED MODELS OFFER INSIGHT, REAL-WORLD SCENARIOS OFTEN DEMAND DETAILED CIRCUIT ANALYSIS AND CALIBRATION DATA.

IN THE CASE OF A 3.25 A READING, UNDERSTANDING

Calculate The Error In The Ammeter Which Reads 3.25 A In a Circuit Having A Series Standard Resistance

Calculate The Error In The Ammeter Which Reads 3.25 A In a Circuit Having A Series Standard Resistance

Related Articles

- [At 2:00 Pm ET, A Customer Enters An Order To Buy GGZ At The Close On The NYSE. GGZ Traded Between 70](#)
- [BestMed Medical Supplies Corporation Sells Medical And Surgical Products and Equipment From More Than](#)
- [Carly And James Share Some Money In A Ratio Of 5:3. Carly Gets 70 More Than James. Work Out How Much](#)

[Back to Home](#)