

The 5.00 A Current Through A 1.50 H Inductor Is Dissipated By A 2.00 Resistor In A Circuit Like That

The 5.00 A Current Through A 1.50 H Inductor Is Dissipated By A 2.00 Resistor In A Circuit Like That is a fundamental concept in electrical engineering that illustrates how energy stored in magnetic fields is converted into heat through resistive elements. Understanding this process involves exploring inductors, resistors, and the dynamics of current decay in RL circuits. This article provides an in-depth analysis of the circuit behavior, the physics behind energy dissipation, and practical implications for designing electrical systems.

Understanding the Basic Components and Circuit Configuration

Inductors and Their Role in Circuits

An inductor is a passive electrical component that stores energy in a magnetic field when current flows through it. Its primary characteristics include inductance (measured in henrys, H), which indicates how much opposition it offers to changes in current. In this case, the inductor has a value of 1.50 H, signifying a substantial ability to oppose sudden changes in current.

Inductors obey Faraday's law of electromagnetic induction, which states that a change in current through the inductor induces an electromotive force (EMF) opposing that change. This property makes inductors essential in filtering, energy storage, and in the transient response of circuits.

Resistor and Power Dissipation

A resistor is a component that opposes the flow of current, converting electrical energy into heat. The resistor in this setup has a resistance of 2.00 ohms, which determines how quickly the energy stored in the inductor's magnetic field is dissipated as heat when the circuit is interrupted or changed.

Typical Circuit Arrangement

The circuit considered here is a simple series RL circuit, where:

- A current of 5.00 A flows through the inductor.

- The inductor (1.50 H) and resistor (2.00 Ω) are connected in series.
- The circuit is either energized initially or is in the process of discharging the stored magnetic energy.

The initial condition assumes that the current has been established at 5.00 A, perhaps after a period of steady operation before switching off or opening the circuit.

Analyzing the Energy Stored in the Inductor

Magnetic Energy Storage

The energy stored in an inductor's magnetic field at any instant is given by the formula:

$$U = \frac{1}{2} L I^2$$

Where:

- U is the stored energy in joules (J),
- L is the inductance (H),
- I is the current (A).

Substituting the given values:

$$U = \frac{1}{2} \times 1.50 \text{ H} \times (5.00 \text{ A})^2 = 0.75 \times 25 = 18.75 \text{ J}$$

This energy represents the magnetic energy stored in the inductor just before the circuit is opened or the current begins to decay.

Implication of Stored Energy

When the circuit is interrupted, this stored energy will dissipate over time through the resistor, converting into heat. The rate and manner of this dissipation depend on the circuit parameters and the nature of the circuit's response.

The Transient Response of the RL Circuit

Discharging the Inductor

When the circuit is suddenly opened (e.g., switch opened), the inductor opposes any rapid change in current. As a result, the current decays exponentially, following the RL circuit transient response:

$$I(t) = I_0 e^{-\frac{R}{L} t}$$

Where:

- I_0 is the initial current (5.00 A),
- R is the resistance (2.00 Ω),
- L is the inductance (1.50 H),
- t is time (s).

The time constant τ for the RL circuit is given by:

$$\tau = \frac{L}{R} = \frac{1.50 \text{ H}}{2.00 \text{ } \Omega} = 0.75 \text{ s}$$

This indicates that the current will decrease to approximately 37% of its initial value after 0.75 seconds.

Power Dissipation Over Time

The instantaneous power dissipated in the resistor during the discharge process is:

$$P(t) = I^2(t) R = (I_0 e^{-\frac{R}{L} t})^2 R$$

Initially, when $t = 0$:

$$P(0) = I_0^2 R = (5.00)^2 \times 2.00 = 25 \times 2 = 50 \text{ W}$$

This is the maximum power dissipated at the instant of switching.

As the current decays, the power dissipated drops exponentially, approaching zero as $t \rightarrow \infty$.

Calculating Total Energy Dissipated as Heat

Energy Dissipation in the Resistor

The total energy initially stored in the magnetic field of the inductor is eventually converted into heat in the resistor. The total energy dissipated, $E_{\text{dissipated}}$, equals the initial energy stored:

$$E_{\text{dissipated}} = U = 18.75 \text{ J}$$

This confirms that all the magnetic energy is converted into thermal energy, assuming an ideal circuit with no other losses.

Verification via Integral of Power Over Time

Alternatively, the total energy dissipated can be calculated by integrating the power over the entire discharging process:

$$E = \int_0^{\infty} P(t) dt = R I_0^2 \int_0^{\infty} e^{-\frac{2R}{L}t} dt$$

Calculating the integral:

$$E = R I_0^2 \times \left[\frac{L}{2R} \right] = \frac{L I_0^2}{2}$$

Plugging in the known values:

$$E = \frac{1.50 \text{ H} \times (5.00)^2}{2} = \frac{1.50 \times 25}{2} = \frac{37.5}{2} = 18.75 \text{ J}$$

This matches the initial energy stored, confirming the consistency of the analysis.

Practical Applications and Considerations

Designing Safe Discharge Paths

In real-world applications, engineers must ensure safe dissipation of stored magnetic energy. Rapid discharges can generate high voltages across the inductor, potentially damaging components or causing arcing. To mitigate this:

- Use snubber circuits or flyback diodes to provide a controlled path for the current.
- Incorporate resistors with appropriate ratings to handle power dissipation.
- Design circuits with sufficient insulation and safety margins.

Energy Efficiency and Heat Management

The heat generated during the energy dissipation process must be managed:

- Select resistors with adequate power ratings (e.g., at least 50 W for the initial dissipation).
- Use heat sinks or cooling methods to prevent overheating.
- Optimize circuit parameters to minimize unnecessary energy loss.

Applications in Inductive Load Control

Understanding how current and energy dissipate in RL circuits is essential in various industries:

- Switching Power Supplies: Managing inductive loads safely during switching operations.
- Motor Drives: Controlling energy in inductive motor windings.
- Pulse Power Systems: Designing circuits that handle rapid energy transfer.

Summary and Key Takeaways

- The initial magnetic energy stored in a 1.50 H inductor with 5.00 A current is 18.75 J.
- When the circuit is opened, this energy is dissipated as heat in the 2.00 Ω resistor, following an exponential decay with a time constant of 0.75 seconds.
- The maximum instantaneous power during discharge is 50 W, decreasing exponentially over time.
- Proper circuit design ensures safe energy dissipation, preventing voltage spikes and managing thermal loads.
- Understanding these principles is vital for designing reliable, efficient electrical systems involving inductors and resistors.

Conclusion

The dissipation of the 5.00 A current through a 1.50 H inductor by a 2.00 Ω resistor exemplifies core concepts of energy storage and transfer in electrical circuits. By analyzing the initial energy stored, the transient response, and the total heat generated, engineers can design safer, more efficient systems. Whether in power supplies, motor control, or pulse circuits, mastering these principles is fundamental to successful electrical engineering practices.

For further reading, consider exploring topics such as RL circuit transient analysis, snubber circuit design, and energy management in inductive loads.

Frequently Asked Questions

What is the power dissipated by the resistor in the circuit?

The power dissipated by the resistor can be calculated using $P = I^2 R$. Substituting $I=5.00$ A and $R=2.00$ Ω , $P = (5.00)^2 \times 2.00 = 25 \times 2 = 50$ W.

How does the inductor's inductance influence the current in the circuit over time?

The inductance (1.50 H) opposes changes in current, meaning that when the circuit is first energized or de-energized, the current will change gradually. The inductance determines the time constant for how quickly the current reaches its steady-state value.

What is the energy stored in the magnetic field of the inductor when the current is 5.00 A?

The energy stored in the inductor is given by $E = (1/2) L I^2$. Substituting $L=1.50$ H and $I=5.00$ A, $E = 0.5 \times 1.50 \times 25 = 0.75 \times 25 = 18.75$ Joules.

If the current through the inductor drops suddenly to zero, how much voltage is induced across the inductor?

The voltage induced across the inductor during a sudden change in current is $V = L (dI/dt)$. Since the change is abrupt, dI/dt is very large, resulting in a very high voltage spike, theoretically approaching infinity in an ideal circuit.

What is the significance of the resistor's value in relation to the inductor's behavior in this circuit?

The resistor's value ($2.00\ \Omega$) determines how quickly the current reaches its steady state and how rapidly the energy stored in the inductor is dissipated as heat. A higher resistance would slow down the current change and reduce the current flow, affecting the circuit's transient response.

Additional Resources

Inductor Power Dissipation: An Expert Examination of the 5.00 A Current Through a 1.50 H Inductor Dissipated by a $2.00\ \Omega$ Resistor

Understanding the intricacies of energy dissipation in electrical circuits is fundamental for engineers, students, and electronics enthusiasts alike. One particularly interesting scenario involves a significant current passing through an inductor and the resulting power loss due to a resistor. In this article, we delve into the specifics of a circuit where a 5.00 A current flows through a 1.50 H inductor, with the energy dissipated across a $2.00\ \Omega$ resistor.

This examination not only clarifies the fundamental principles underlying inductive energy dissipation but also provides a comprehensive analysis of the key calculations involved, practical implications, and real-world applications.

Understanding the Circuit Components and Setup

Before diving into calculations, it's crucial to understand the core components involved and their roles within the circuit.

The Inductor: 1.50 H

An inductor is a passive electronic component that opposes changes in current by storing energy in its magnetic field. The inductance value, measured in henrys (H), indicates how much magnetic flux is generated per unit current. In this case:

- Inductance (L): 1.50 H

This relatively large inductance suggests the device is capable of storing a

significant amount of magnetic energy when current flows through it.

The Resistor: 2.00 Ω

The resistor acts as an energy dissipator in the circuit. Its resistance value determines how much electrical energy is converted into heat:

- Resistance (R): 2.00 Ω

The resistor's role is critical in defining the power dissipated from the system, especially when the current is steady or changing.

The Steady-State Current: 5.00 A

The specified current of 5.00 A suggests the circuit has reached a steady state where the current remains constant over time, or we're analyzing a snapshot where transient effects are negligible.

Theoretical Foundations: Power Dissipation in Inductive Circuits

The core concept here revolves around how energy stored in an inductor is dissipated through a resistor, and the principles governing this process.

Magnetic Energy Stored in the Inductor

The energy (U) stored in an inductor with current (I) is given by:

$$U = \frac{1}{2} L I^2$$

Where:

- (L) is the inductance (H)
- (I) is the current (A)

This energy can be released as heat in the resistor once the circuit is configured to allow current decay, or it can be considered in the context of energy transfer and dissipation.

Power Dissipation in the Resistor

When a current flows through a resistor, the power (P) dissipated as heat is:

$$P = I^2 R$$

This is the instantaneous power at any given moment, assuming the current remains constant.

Calculating Power Dissipation: Step-by-Step Analysis

The main objective is to determine the power dissipated by the resistor, given the current and resistance values. We will also examine the energy stored in the inductor and consider dynamic effects.

Steady-State Power Dissipation

Given the steady current:

$$I = 5.00 \text{ A}$$
$$R = 2.00 \text{ } \Omega$$

The power dissipated in the resistor is:

$$P = I^2 R = (5.00)^2 \times 2.00 = 25 \times 2 = 50 \text{ W}$$

Result: The resistor dissipates 50 Watts of power at this current level.

This calculation assumes the circuit is in a steady state where the current is constant. In such a case, the inductor's energy storage doesn't directly contribute to the instantaneous power dissipation but plays a role during transient conditions.

Energy Stored in the Inductor

Although the immediate power loss is 50 W, understanding the energy stored provides insight into the circuit's dynamics:

$$U = \frac{1}{2} L I^2 = \frac{1}{2} \times 1.50 \times (5.00)^2 = 0.75 \times 25 = 18.75 \text{ J}$$

Interpretation: The inductor stores approximately 18.75 Joules of magnetic energy when the current is 5.00 A.

Transient Response and Energy Dissipation Dynamics

While the steady-state power calculation offers a snapshot, the true dynamics involve how energy stored in the inductor dissipates over time, especially during switching events or circuit interruptions.

Decay of Current and Power Dissipation Over Time

Suppose the circuit is suddenly disconnected or switched off. The inductor's stored energy will cause the current to decay exponentially, governed by the circuit's time constant.

The current decay in an RL circuit follows:

$$I(t) = I_0 e^{-\frac{R}{L} t}$$

Where:

- $I_0 = 5.00 \text{ A}$
- $R = 2.00 \text{ } \Omega$
- $L = 1.50 \text{ H}$

The time constant (τ) :

$$\tau = \frac{L}{R} = \frac{1.50}{2.00} = 0.75 \text{ s}$$

This indicates the current drops to approximately 37% of its initial value after 0.75 seconds.

The power dissipated during decay:

$$P(t) = I(t)^2 R = \left(I_0 e^{-\frac{R}{L} t} \right)^2 R$$

which decreases exponentially, converting the magnetic energy into heat over time.

Implications for Circuit Design and Safety

Understanding the power dissipation and energy decay is vital for:

- Component Selection: Ensuring resistors can handle maximum power dissipation.
- Thermal Management: Adequate heat sinks or cooling systems.
- Transient Protection: Incorporating snubbers or diodes to manage voltage spikes during switching.

Practical Considerations and Real-World Applications

While theoretical calculations provide clarity, real-world applications demand consideration of additional factors:

Efficiency and Energy Losses

The dissipation of 50 W purely as heat illustrates the inevitable energy loss in resistive elements. Engineers strive to minimize such losses in high-power circuits through:

- Using superconducting materials (where feasible).
- Employing low-resistance conductors.
- Optimizing circuit topology.

Applications of Inductive Power Dissipation

Understanding how energy dissipates in inductive-resistive circuits is critical in:

- Power Supplies: Managing transient responses and energy recovery.
- Motor Control: Handling inductance-related energy during switching.
- Electromagnetic Devices: Designing inductors and resistors for desired energy storage and dissipation characteristics.
- Inductive Heating: Harnessing resistive losses in inductor coils for heating applications.

Safety and Reliability

High power dissipation demands careful circuit design to prevent overheating, component failure, and ensure long-term reliability. Proper insulation, heat sinking, and safety margins are indispensable.

Summary and Final Thoughts

Analyzing the circuit where a 5.00 A current flows through a 1.50 H inductor with energy dissipated by a 2.00 Ω resistor reveals several key insights:

- The resistor dissipates a significant 50 W of power at steady state.
- The inductor stores approximately 18.75 Joules of magnetic energy at this current.
- Transient behaviors involve exponential decay of current and energy release.
- Practical applications require careful thermal and safety considerations.

This comprehensive review underscores the importance of understanding both the static and dynamic aspects of inductive circuits, especially in high-current, high-energy scenarios. Whether designing power systems, motors, or electromagnetic devices, mastering these principles ensures efficiency, safety, and optimal performance.

In conclusion, the dissipation of current energy in inductive-resistive circuits is a fundamental concept with wide-ranging implications in electronics and electrical engineering. By grasping the calculations and real-world considerations outlined here, engineers and enthusiasts can better design, analyze, and troubleshoot systems that rely on the delicate interplay of inductance and resistance.

The 5 00 A Current Through A 1 50 H Inductor Is Dissipated By A 2 00 Resistor In A Circuit Like That

The 5 00 A Current Through A 1 50 H Inductor Is Dissipated By A 2 00 Resistor In A Circuit Like That

Related Articles

- [Suppose That For Health Reasons, The Government Of The Nation Of Ironia Wants To Increase The Amount](#)
- [Read The Passage.\(1\) I Think That Schools Should Switch From Using Paper Textbooks To Using Computer](#)
- [Test The Series Below For Convergence. \$3 + \frac{N - 1}{n} + \frac{1}{4} + 2n\$ \$N=2\$ A. The Series Is Select An Answer B.](#)

[Back to Home](#)