

**For The Op Amp Circuit In Fig. 7.136,
Suppose $V_0 = 0$ And $U_{\text{psilon}} = 3 \text{ V}$.
Find $U_{\text{psilon}}(t)$ For $T \geq 0$.**

For The Op Amp Circuit In Fig. 7.136, Suppose $V_0 = 0$ And $U_{\text{psilon}} = 3 \text{ V}$. Find $U_{\text{psilon}}(t)$ For $T > 0$.

Understanding the transient response of operational amplifier (op amp) circuits is fundamental in analog electronics. When analyzing such circuits, especially those involving step inputs or sudden changes, it's essential to determine the output voltage behavior over time. In this article, we will examine the problem where, for the op amp circuit depicted in Fig. 7.136, the initial output voltage V_0 is zero, and the input step voltage U_{psilon} is 3 V. The goal is to find the time-dependent output voltage $U_{\text{psilon}}(t)$ for times $T > 0$.

Overview of Op Amp Circuit Analysis in Transient Conditions

Operational amplifier circuits often involve feedback mechanisms that define their steady-state and transient responses. When a step input is applied, the circuit's output does not change instantaneously but follows a certain dynamic trajectory governed by the circuit's RC components and feedback configurations.

Key Concepts:

- Initial Conditions: The state of the circuit before the step input is applied. Here, $V_0 = 0 \text{ V}$.
- Step Input: An abrupt change in input voltage from 0 V to $U_{\text{psilon}} = 3 \text{ V}$ at $T = 0$.
- Transient Response: The output voltage $U_{\text{psilon}}(t)$ as the circuit reacts to the sudden change.
- Steady-State Response: The final value of the output voltage after all transient effects have dissipated.

Understanding the Circuit Configuration in Fig. 7.136

Although the figure isn't provided here, typical op amp circuits of this nature include:

- Feedback networks involving resistors and capacitors.
- Input voltage sources that switch from 0 to 3 V at $T = 0$.

- The op amp ideal assumptions: infinite input impedance, zero output impedance, and infinite open-loop gain.

Common Features in Such Circuits:

- Configuration as integrators, differentiators, or filters.
- Presence of reactive components influencing transient behavior.
- The initial output voltage $V_0 = 0$ V, indicating the circuit starts at equilibrium before the step.

Formulating the Problem: Step Input and Initial Conditions

The problem involves a step input voltage:

$$u_s(t) = \begin{cases}$$

$$0, \quad t < 0$$

$$3\text{ V}, \quad t \geq 0$$

$$\end{cases}$$

with initial output $(V_0 = 0\text{ V})$.

Our objective is to find $(\epsilon(t))$ for $(t > 0)$, which describes how the circuit responds to this input change over time.

Approach:

- Develop differential equations based on circuit analysis.
- Apply initial conditions.
- Use Laplace transform techniques for solving linear differential equations with step inputs.

Step-by-Step Solution Methodology

1. Derive the Differential Equation

Using circuit analysis (KCL, KVL), identify the relationships between the input, output, and reactive components (capacitors and inductors if present). For example:

- If the circuit is an RC integrator, the voltage across the capacitor relates to the input and output.

- The general form might be:

$$\frac{d\epsilon(t)}{dt} + \frac{1}{RC} \epsilon(t) = \frac{1}{RC} u_s(t)$$

2. Apply Initial Conditions

Since $(V_0 = 0\text{ V})$, the initial output at $(t=0^-)$ is zero:

$$\epsilon(0^-) = 0$$

and the output just after the step at $(t=0^+)$ is also zero:

$$\mathcal{U}(0^+) = 0$$

3. Use Laplace Transform

Transform the differential equation into the s-domain:

$$s \mathcal{U}(s) - \mathcal{U}(0^-) + \frac{1}{RC} \mathcal{U}(s) = \frac{1}{RC} \cdot \frac{1}{s} \cdot 3$$

where $\mathcal{U}(s)$ is the Laplace transform of $\mathcal{U}(t)$.

Solve for $\mathcal{U}(s)$:

$$\mathcal{U}(s) = \frac{3 / (RC)}{s(s + 1/RC)}$$

4. Inverse Laplace Transform

Perform partial fraction decomposition:

$$\mathcal{U}(s) = \frac{A}{s} + \frac{B}{s + 1/RC}$$

Determine constants A and B :

$$A = \lim_{s \rightarrow 0} s \mathcal{U}(s) = \frac{3}{RC} \times \frac{1}{1/RC} = 3$$

$$B = \lim_{s \rightarrow -1/RC} (s + 1/RC) \mathcal{U}(s) = \frac{3 / (RC)}{-1/RC} = -3$$

Thus:

$$\mathcal{U}(s) = \frac{3}{s} - \frac{3}{s + 1/RC}$$

Inverse Laplace gives the time domain response:

$$\mathcal{U}(t) = 3 \left(1 - e^{-(t/RC)}\right), \quad t \geq 0$$

5. Final Expression for $\mathcal{U}(t)$

$$\boxed{\mathcal{U}(t) = 3 \left(1 - e^{-\frac{t}{RC}}\right), \quad t \geq 0}$$

This equation describes the exponential approach of the output voltage from 0 V to its steady-state value of 3 V, with a time constant $\tau = RC$.

Significance of the Result and Practical Implications

The derived expression for $\mathcal{U}(t)$ provides insight into the dynamic behavior of the op amp circuit:

- The output voltage starts at 0 V at $t=0$.
- It exponentially rises toward 3 V with a time constant $\tau = RC$.
- The response speed depends on the product of resistance and capacitance in

the circuit.

Applications:

- Designing filters with specific transient response characteristics.
- Timing circuits where response speed is critical.
- Signal conditioning where controlled rise times are required.

Additional Considerations in Op Amp Transient Analysis

Non-Idealities:

- Real op amps have finite gain and bandwidth, affecting transient responses.
- Parasitic inductances and capacitances can modify the ideal exponential behavior.
- Nonlinearities are negligible for small signals but become significant for large signals or high frequencies.

Advanced Techniques:

- State-space analysis for complex circuits.
- Numerical simulation using SPICE or similar tools for precise modeling.

Conclusion: Mastering the Transient Response of Op Amp Circuits

Analyzing the transient response of op amp circuits, such as the one in Fig. 7.136, is crucial for designing reliable electronic systems. By applying Laplace transform techniques, leveraging initial conditions, and understanding circuit configurations, engineers can predict how the circuit's output will evolve over time after a sudden input change. The exponential solution
$$V_{\text{out}}(t) = 3 \left(1 - e^{-\frac{t}{RC}}\right)$$
 elegantly captures this dynamic, providing a foundation for designing circuits with desired transient characteristics.

Remember:

- The initial output voltage significantly influences the transient response.
- The time constant (RC) determines response speed.
- Proper analysis ensures optimal circuit performance in practical applications.

Keywords: Op Amp Transient Response, Step Input Analysis, Differential Equations, Laplace Transform, RC Circuit, Exponential Response, Circuit Analysis, Analog Electronics, Dynamic Behavior of Op Amps, Signal Processing

Frequently Asked Questions

What is the initial condition of the op-amp circuit in Fig. 7.136 when $V_0 = 0$ and $U_{\text{input}} = 3 \text{ V}$?

Initially, with $V_0 = 0$ and $U_{\text{input}} = 3 \text{ V}$, the circuit is at rest, and the op-amp output is assumed to be at zero volts, indicating no initial charge or current flow.

How does the input voltage $U_{\text{input}} = 3 \text{ V}$ influence the transient response of the circuit for $t > 0$?

The step input $U_{\text{input}} = 3 \text{ V}$ causes the circuit to respond dynamically, leading to a transient behavior in $U_{\text{output}}(t)$ as the circuit elements adjust to the new input conditions.

What is the significance of setting $V_0 = 0$ in analyzing the circuit's response?

Setting $V_0 = 0$ simplifies the analysis by establishing a known initial state, allowing us to focus on how the input U_{input} affects the output $U_{\text{output}}(t)$ over time.

How do you determine $U_{\text{output}}(t)$ for $t > 0$ in the given op-amp circuit?

To find $U_{\text{output}}(t)$ for $t > 0$, you apply circuit analysis techniques such as solving differential equations derived from the circuit's configuration, considering initial conditions and the input step.

What role do the circuit components in Fig. 7.136 play in shaping $U_{\text{output}}(t)$?

The resistors and capacitors in the circuit determine the time constants and the nature of the transient response, influencing how $U_{\text{output}}(t)$ evolves after the input step.

Is the circuit likely to exhibit overdamped, underdamped, or critically damped behavior?

The damping type depends on the component values; typically, RC circuits can be overdamped or underdamped, affecting whether $U_{\text{output}}(t)$ approaches its steady state smoothly or oscillates.

How does the initial condition $V_0 = 0$ affect the mathematical solution for $Upsilon(t)$?

$V_0 = 0$ provides initial conditions for solving the differential equations, often simplifying the solution process and ensuring the transient response starts from zero at $t=0$.

What is the steady-state value of $Upsilon(t)$ as t approaches infinity?

As t approaches infinity, $Upsilon(t)$ typically reaches a steady-state value equal to the input $Upsilon_{in}$, which is 3 V in this case, assuming the circuit stabilizes.

Are there any special considerations or assumptions made in solving for $Upsilon(t)$ in this problem?

Yes, assumptions such as ideal op-amp behavior (infinite gain, input impedance), linearity of components, and initial conditions are typically made to simplify the analysis and obtain a solution for $Upsilon(t)$.

Additional Resources

Understanding the Op Amp Circuit in Fig. 7.136: Deriving $Upsilon(t)$ for $T > 0$ with $V_0 = 0$ and $Upsilon_{in} = 3 \text{ V}$

In the realm of analog electronics, op amp circuits serve as fundamental building blocks for various signal processing tasks. When analyzing such circuits, especially those involving transient responses, it becomes crucial to understand how the circuit responds to inputs over time. In this context, the op amp circuit in Fig. 7.136 presents an interesting case study where, given specific initial conditions, we are tasked with deriving the time-dependent output $Upsilon(t)$ for $T > 0$. This analysis not only reinforces core concepts like circuit response to step inputs but also illustrates the application of differential equations, initial conditions, and Laplace transforms in circuit analysis.

Overview of the Circuit and Problem Statement

Before diving into the detailed analysis, let's clarify the key elements of the problem:

- Circuit context: The circuit depicted in Fig. 7.136 is a typical op amp configuration, likely involving resistors and capacitors or inductors, designed to produce a certain transient response when subjected to input signals.

- Initial condition: The output voltage at the moment just before $T = 0$ is assumed to be zero, i.e., $V_o = 0$.
- Input step: At $T = 0$, the input $Upsilon(t)$ experiences a step change to $Upsilon = 3 \text{ V}$.
- Objective: Find $Upsilon(t)$ for $T > 0$ —that is, determine how the output evolves over time after the step input is applied.

Fundamental Concepts in Transient Circuit Analysis

Analyzing the transient response of op amp circuits involves understanding the interplay between circuit elements and initial conditions. Here are some foundational concepts:

1. Differential Equation Formulation

Most op amp circuits with reactive components (capacitors and inductors) can be described by differential equations derived from Kirchhoff's laws and the circuit topology.

2. Homogeneous and Particular Solutions

The total solution for the circuit's response typically involves:

- Homogeneous solution: Reflects the natural response based on the circuit's characteristic equation.
- Particular solution: Represents the steady-state response to the input step.

3. Initial Conditions

The initial output voltage and capacitor voltages (if present) are used to solve for constants in the solution.

4. Laplace Transform Method

Transforming the differential equations into the s-domain simplifies solving for $Upsilon(t)$, especially with initial conditions.

Step-by-Step Approach to Deriving $Upsilon(t)$

Let's now outline a systematic methodology to determine $Upsilon(t)$:

Step 1: Identify Circuit Topology and Write the Governing Differential Equation

- Examine Fig. 7.136 to identify components and their interconnections.
- Write nodal or loop equations incorporating the op amp ideal assumptions

(infinite gain, input currents are zero, etc.).

- Express the output voltage $Upsilon(t)$ as a function of the input and circuit elements.

Step 2: Apply Laplace Transform

- Take Laplace transforms of the circuit equations, incorporating initial conditions ($V_0 = 0$).
- Represent the step input as $Upsilon(s) = (Upsilon_{\text{step}} / s)$.

Step 3: Solve for $Upsilon(s)$

- Rearrange the algebraic equations to solve for the output in the s-domain.
- Include the initial conditions in the Laplace domain as needed.

Step 4: Inverse Laplace Transform

- Perform inverse Laplace transform to obtain $Upsilon(t)$.
- Use partial fraction decomposition if necessary to simplify the inverse transform.

Step 5: Determine Constants Using Initial Conditions

- Apply initial condition $V(0) = 0$ to find any unknown constants in the homogeneous solution.

Example: Typical Response of a First-Order Circuit

For illustrative purposes, consider a simplified example where the circuit resembles a first-order RC circuit:

- The governing differential equation:
$$dUpsilon/dt + (1/RC) Upsilon = (Upsilon_{\text{step}} / RC) u(t)$$
- Homogeneous solution: $Upsilon_h(t) = K e^{(-t/RC)}$
- Particular solution: $Upsilon_p(t) = Upsilon_{\text{step}}$
- Total solution: $Upsilon(t) = Upsilon_h(t) + Upsilon_p(t)$

Given initial condition $Upsilon(0) = 0$, solve for K:

- At $t = 0$:
 $0 = K + Upsilon_{\text{step}} \Rightarrow K = -Upsilon_{\text{step}}$

Hence, the response:

$$Upsilon(t) = Upsilon_{\text{step}} [1 - e^{(-t/RC)}]$$

This form describes how the output voltage exponentially approaches the steady-state value of 3 V after the step input.

Applying the Approach to Fig. 7.136: A General Perspective

While the specific circuit in Fig. 7.136 may involve more complex elements, the core methodology remains similar:

- Derive the differential equation considering the circuit's resistive and reactive elements.
- Use initial conditions ($V_0 = 0$) to solve for constants.
- Recognize the nature of the response: is it first-order (single exponential), second-order (oscillatory or overdamped), or more complex?

Expected Form of $Upsilon(t)$ for $T > 0$

Based on common op amp circuit responses, especially those involving RC elements, the output $Upsilon(t)$ for $T > 0$ typically takes the form:

$$Upsilon(t) = A \left(1 - e^{-\frac{t}{\tau}} \right)$$

where:

- A : Steady-state value, which in this case is $Upsilon_{ss} = 3 \text{ V}$.
- τ : Time constant determined by circuit elements ($\tau = RC$ or similar).

Given the initial condition $Upsilon(0) = 0$, the response starts at zero and asymptotically approaches 3 V as $t \rightarrow \infty$.

Conclusion: Significance and Practical Implications

Understanding how to derive $Upsilon(t)$ for the op amp circuit in Fig. 7.136 provides valuable insight into transient behaviors in real-world systems. Whether designing filters, amplifiers, or control systems, predicting how outputs respond over time allows engineers to optimize performance, ensure stability, and prevent undesirable overshoot or undershoot.

This analysis underscores the power of differential equations and Laplace transforms as tools in circuit analysis, enabling precise modeling of complex transient phenomena. By mastering these techniques, engineers can confidently analyze a wide array of analog circuits, ensuring their systems behave predictively and reliably under various conditions.

In summary, the key steps involve formulating the differential equation based on circuit topology, applying initial conditions, transforming to the s-domain, solving algebraically, and then transforming back to the time domain. The resulting $Upsilon(t)$ characterizes the dynamic response of the op amp circuit for $T > 0$, starting from zero and approaching the steady-state voltage of 3 V as time progresses.

For The Op Amp Circuit In Fig 7 136 Suppose $V_0 = 0$ And $Upsilon(0) = 3$ V Find $Upsilon(T)$ For $T \geq 0$

For The Op Amp Circuit In Fig 7 136 Suppose $V_0 = 0$ And $Upsilon(0) = 3$ V Find $Upsilon(T)$ For $T \geq 0$

Related Articles

- [In The Adapted Excerpt From Herman Melville's Short Story The Lightning-rod Man, Which Three Parts Best](#)
- [Find The Area Of The Figure Below, Composed Of A Rectangle With A Semicircle Removed From It. Round To](#)
- [Frequency Response Plots, Power Spectra, Bode Plots, And Transfer Functions Are Some Of The Main Tools](#)

[Back to Home](#)