

A Battery Has An Emf Of V And An Internal Resistance Of R , What Resistance R , When Connected Across The

A Battery Has An Emf Of V And An Internal Resistance Of R , What Resistance R , When Connected Across The a load resistor? This question is fundamental in understanding how batteries operate within electrical circuits and how their internal characteristics influence the overall performance. In this article, we will explore the concepts of electromotive force (emf), internal resistance, and how to determine the appropriate external resistance to optimize battery performance. We will also delve into practical applications and considerations for designing circuits involving batteries.

Understanding Emf and Internal Resistance

What is Electromotive Force (Emf)?

Electromotive force, commonly denoted as V in equations, is the maximum potential difference generated by a battery or power source when no current is flowing. It is measured in volts (V) and represents the energy provided per unit charge by the battery's chemical reactions.

Internal Resistance of a Battery

Every real battery exhibits some internal resistance, R , which is due to the materials and processes within the battery. Internal resistance causes voltage drops within the battery itself when current flows and results in energy losses as heat.

Key points about internal resistance:

- It reduces the effective voltage delivered to the external circuit.
- It causes the terminal voltage to be less than emf when current is drawn.
- It impacts battery efficiency and lifespan.

Modeling a Battery: The Equivalent Circuit

To analyze how a battery behaves when connected to an external resistor, engineers use an equivalent circuit model:

- Emf Source (V): Represents the ideal voltage of the battery.
- Internal Resistance (R): Models the internal losses within the battery.
- External Resistance (R_{load}): The resistor connected across the battery terminals.

The circuit resembles a voltage source V in series with an internal resistor R , connected across the load resistor R_{load} .

Determining the Resistance R When Connected Across the Battery

Suppose you want to choose an external resistance R for a load connected to a battery with emf V and internal resistance R . The goal may be to maximize power transfer, ensure safe operation, or optimize efficiency.

Maximum Power Transfer Theorem

A fundamental principle in circuit theory states:

> To transfer maximum power from a source to a load, the load resistance R_{load} should be equal to the internal resistance R of the source.

Mathematically:

$$R = R_{\text{load}}$$

Implication:

- When $R = R$, the power delivered to the load is maximized.
- The terminal voltage V_{terminal} under this condition is:

$$V_{\text{terminal}} = V \times (R / (R + R)) = V / 2$$

- The current through the circuit is:

$$I = V / (R + R) = V / (2R)$$

- The power dissipated in R_{load} is:

$$P = I^2 \times R = (V^2) / (4R)$$

Note: While maximum power transfer is useful in certain contexts, it is often not the most efficient method, especially in power supply applications where efficiency is critical.

Calculating Resistance R for a Given Current or Voltage

If the goal is to ensure a specific current I or terminal voltage V_t , you can derive R as follows:

- From Ohm's Law:

$$V_t = V - I \times R$$

- Rearranged to find R :

$$R = (V - V_t) / I$$

Example:

Suppose the battery has a V of 12 V, an internal resistance R of 0.5 Ω , and you want a load current of 2 A:

$$R_{\text{load}} = (V - I \times R) / I = (12 - 2 \times 0.5) / 2 = (12 - 1) / 2 = 11 / 2 = 5.5 \Omega$$

Thus, connecting a 5.5 Ω resistor across the battery will provide a 2 A current, considering the internal resistance.

Practical Applications and Considerations

Battery Selection in Circuits

Choosing the correct external resistance R is essential in designing circuits for:

- Power delivery: Ensuring the load receives adequate power without overloading the battery.
- Battery longevity: Avoiding excessive current that can lead to overheating or damage.
- Efficiency optimization: Balancing power transfer with energy conservation.

Impact of Internal Resistance on Battery Performance

As internal resistance increases (which can happen with aging or high current draw), the voltage available to the load decreases, impacting device operation.

Strategies to mitigate internal resistance effects:

- Use batteries with lower internal resistance.
- Limit current draw to prevent excessive voltage drops.
- Avoid overly low load resistances that cause high current flow.

Designing for Safety and Reliability

When selecting R, consider the following:

- Ensure the resistor can handle the power dissipation, calculated as $P = I^2 R$.
- Use resistors with appropriate voltage and temperature ratings.
- Account for temperature effects, as resistance can vary with temperature.

Summary and Key Takeaways

- The internal resistance of a battery impacts how it behaves under load.
- To maximize power transfer, set the load resistance equal to the internal resistance.
- The terminal voltage decreases as current increases, following Ohm's law.
- Practical circuit design requires balancing power needs, efficiency, safety, and battery health.
- Proper selection and calculation of resistance R ensure optimal performance and longevity of the battery.

Conclusion

Understanding the relationship between emf, internal resistance, and external load resistance is fundamental in electrical engineering and circuit design. Whether aiming for maximum power transfer or efficiency, calculating and choosing the appropriate resistance R when connecting a battery across a load is crucial. By considering the internal characteristics of the battery and the application's requirements, engineers and technicians can optimize circuit performance, extend battery life, and ensure safe operation.

References:

- Basic Electricity and Electronics Textbooks
- Circuit Theory and Analysis Resources
- Battery Technology and Performance Studies

Frequently Asked Questions

A battery has an emf of V and an internal resistance R . What should be the external resistance R_{ext} to ensure maximum power transfer when connected across the battery?

To achieve maximum power transfer, the external resistance R_{ext} should be equal to the internal resistance R of the battery.

How does the internal resistance R of a battery affect the current when connected across a resistor R_{ext} ?

The internal resistance R reduces the net current flowing through the external resistor R_{ext} , according to Ohm's law: $I = V / (R_{\text{ext}} + R)$.

If a battery has emf V and internal resistance R , what is the terminal voltage when connected to a load resistance R_{load} ?

The terminal voltage $V_{\text{terminal}} = V - I R$, where $I = V / (R_{\text{load}} + R)$.

When connected across a resistor R_{ext} , what is the power dissipated in the internal resistance R of the battery?

The power dissipated in the internal resistance is $P_R = I^2 R$, where $I = V / (R_{\text{ext}} + R)$.

What is the effect of increasing the external resistance R_{ext} on the current and power output of the battery?

Increasing R_{ext} decreases the current I but can increase the power delivered to the load up to a point, especially when R_{ext} equals R for maximum power transfer.

How can we determine the internal resistance R of a battery experimentally?

By measuring the terminal voltage and current for different load resistances and using $V = \text{emf} - I R$ to calculate R from the slope of V versus I graph.

What is the significance of the internal resistance R in the overall performance of a battery?

Internal resistance R causes voltage drops within the battery, reducing the terminal voltage under load and leading to energy losses as heat, thereby affecting efficiency and performance.

If the emf of the battery is V and internal resistance R , what is the maximum power that can be delivered to a load?

Maximum power is delivered when the load resistance R_{load} equals R , and the maximum power is $P_{\text{max}} = V^2 / (4 R)$.

Why does the terminal voltage of a battery decrease when a load is connected, assuming internal resistance R ?

Because the current I flowing through the internal resistance causes a voltage drop ($I R$), reducing the terminal voltage below the emf V .

When connecting a resistor R across a battery with emf V and internal resistance R , how do you calculate the current flowing through the circuit?

The current $I = V / (R + R)$, where R is the internal resistance and the external resistor; effectively, $I = V / (R_{\text{external}} + R_{\text{internal}})$.

Additional Resources

A Battery Has An emf of V and an Internal Resistance of R , What Resistance R , When Connected Across The

Introduction

In the realm of electrical circuits and energy transfer, understanding the behavior of batteries under various load conditions is crucial. A common

question faced by students, engineers, and hobbyists alike is: Given a battery with an electromotive force (emf) V and an internal resistance R , what external resistance R_0 should be connected across the battery to achieve a specific operational goal? This inquiry touches upon fundamental concepts in circuit theory, power transfer, and real-world applications, making it a rich subject for detailed exploration.

This article aims to dissect this problem thoroughly, examining the underlying principles, mathematical relationships, practical considerations, and implications. We will analyze the scenario from multiple angles, including theoretical foundations, practical constraints, and optimization strategies, providing a comprehensive understanding suitable for review and scholarly analysis.

Understanding the Basic Concepts

Electromotive Force (emf) and Internal Resistance

A battery can be modeled as an ideal emf source V in series with an internal resistance R . The emf V represents the maximum potential difference the battery could deliver if no current flows. The internal resistance R accounts for the internal energy losses due to chemical and physical processes within the battery.

When the battery supplies current, I , the actual terminal voltage V_t drops below emf V due to the internal resistance:

$$V_t = V - IR$$

The power delivered to an external resistor R_0 (denoted R in the problem statement) is then:

$$P_{\text{out}} = I^2 R_0$$

The current I in the circuit, considering the internal resistance, is:

$$I = \frac{V}{R + R_0}$$

The Fundamental Question

The key question posed is: "What resistance R_0 should be connected across the

battery?"

While the initial statement suggests R is known, it often implies that R_0 (the external resistance) is the variable to be determined, or vice versa. For clarity, we interpret the question as:

> Given a battery with emf V and internal resistance R , what external resistance R_0 should be connected across it to optimize a specific performance criterion?

Common objectives include:

- Maximizing power transfer to R_0
- Achieving a particular terminal voltage
- Minimizing energy loss
- Ensuring safe operation

In this discussion, we will focus on the classic problem of maximizing power transfer, which is fundamental in circuit analysis and design.

The Maximum Power Transfer Theorem

Statement of the Theorem

The Maximum Power Transfer Theorem states that:

> To transfer the maximum possible power from a source with emf V and internal resistance R to a load R_0 , the load resistance must be equal to the internal resistance of the source:

$$\begin{aligned} & \backslash[\\ & R_{0} = R \\ & \backslash] \end{aligned}$$

This condition ensures that the power delivered to R_0 is maximized, though it also implies that half of the power is dissipated internally, which is inefficient from an energy perspective but optimal for power transfer purposes.

Deriving the Optimal External Resistance R_0

Power as a Function of R_0

The power delivered to R_0 is:

$$\begin{aligned} & \backslash[\\ & P_{\text{out}} = I^2 R_0 \end{aligned}$$

\]

Substituting I:

$$\begin{aligned} & \left[\right. \\ I &= \frac{V}{R + R_{\{0\}}} \\ & \left. \right] \end{aligned}$$

Thus,

$$\begin{aligned} & \left[\right. \\ P_{\text{out}} &= \left(\frac{V}{R + R_{\{0\}}} \right)^2 R_{\{0\}} \\ & \left. \right] \end{aligned}$$

Maximizing Power

To find the R_0 that maximizes P_{out} , differentiate with respect to R_0 and set the derivative to zero:

$$\begin{aligned} & \left[\right. \\ \frac{d}{d R_{\{0\}}} P_{\text{out}} &= 0 \\ & \left. \right] \end{aligned}$$

Calculating the derivative:

$$\begin{aligned} & \left[\right. \\ \frac{d}{d R_{\{0\}}} \left[\frac{V^2 R_{\{0\}}}{(R + R_{\{0\}})^2} \right] &= 0 \\ & \left. \right] \end{aligned}$$

Applying the quotient rule:

$$\begin{aligned} & \left[\right. \\ V^2 \frac{(R + R_{\{0\}})^2 - R_{\{0\}} \cdot 2(R + R_{\{0\}})}{(R + R_{\{0\}})^4} &= 0 \\ & \left. \right] \end{aligned}$$

Simplify numerator:

$$\begin{aligned} & \left[\right. \\ (R + R_{\{0\}})^2 - 2 R_{\{0\}} (R + R_{\{0\}}) &= 0 \\ & \left. \right] \end{aligned}$$

Factor out $(R + R_{\{0\}})$:

$$\begin{aligned} & \left[\right. \\ (R + R_{\{0\}}) \left[(R + R_{\{0\}}) - 2 R_{\{0\}} \right] &= 0 \\ & \left. \right] \end{aligned}$$

Since $(R + R_0) \neq 0$:

$$\begin{aligned} & \left[\right. \\ (R + R_{\{0\}}) - 2 R_{\{0\}} &= 0 \end{aligned}$$

\]

$$\begin{aligned} & \left[\right. \\ & R + R_{\{0\}} = 2 R_{\{0\}} \\ & \left. \right] \end{aligned}$$

$$\begin{aligned} & \left[\right. \\ & R = R_{\{0\}} \\ & \left. \right] \end{aligned}$$

Result: The power delivered to R_0 is maximized when:

$$\begin{aligned} & \left[\right. \\ & \boxed{R_{\{0\}} = R} \\ & \left. \right] \end{aligned}$$

This confirms the classic maximum power transfer condition.

Practical Implications and Limitations

Power Transfer vs. Efficiency

While matching R_0 to R maximizes power transfer, this does not mean the most efficient energy use. The efficiency η , defined as:

$$\begin{aligned} & \left[\right. \\ & \eta = \frac{\text{Power delivered to } R_{\{0\}}}{\text{Total power supplied by the battery}} = \frac{I^2 R_{\{0\}}}{V I} \\ & \left. \right] \end{aligned}$$

simplifies to:

$$\begin{aligned} & \left[\right. \\ & \eta = \frac{R_{\{0\}}}{R + R_{\{0\}}} \\ & \left. \right] \end{aligned}$$

At $R_0 = R$, efficiency is:

$$\begin{aligned} & \left[\right. \\ & \eta = \frac{R}{2 R} = 0.5 \\ & \left. \right] \end{aligned}$$

meaning only 50% of the power supplied by the battery reaches the external load, with the rest dissipated internally.

Real-World Constraints

In practical applications, the ideal R_0 matching R may not be desirable due to:

- Battery lifespan considerations: Excessive internal dissipation can degrade the battery.
- Voltage regulation needs: Sometimes, a specific terminal voltage is necessary, requiring R_0 to be chosen differently.
- Safety and reliability: Excessive current or heat dissipation poses hazards.
- Efficiency priorities: Often, optimizing for maximum efficiency (minimizing internal losses) is more critical than maximum power transfer.

Extending the Analysis to Different Objectives

Achieving a Specific Terminal Voltage

Suppose the goal is to maintain a particular terminal voltage V_t across R_0 :

$$\begin{aligned} & \backslash[\\ V_t &= V - IR \\ & \backslash] \end{aligned}$$

And

$$\begin{aligned} & \backslash[\\ I &= \frac{V}{R + R_0} \\ & \backslash] \end{aligned}$$

then,

$$\begin{aligned} & \backslash[\\ V_t &= V - R \frac{V}{R + R_0} = V \left(1 - \frac{R}{R + R_0}\right) = \\ & V \frac{R_0}{R + R_0} \\ & \backslash] \end{aligned}$$

To maintain a desired V_t :

$$\begin{aligned} & \backslash[\\ V_t &= V \frac{R_0}{R + R_0} \\ & \backslash] \end{aligned}$$

which leads to:

$$\begin{aligned} & \backslash[\\ R_0 &= \frac{V_t}{V - V_t} R \\ & \backslash] \end{aligned}$$

This formula allows selecting R_0 to achieve a specified terminal voltage, considering the internal resistance R .

Practical Design Considerations

Selecting R_0 for Optimal Performance

In designing circuits and devices powered by batteries, engineers often consider:

- Maximum power transfer for testing or signal purposes
- Efficiency for energy conservation
- Voltage regulation for consistent operation

Depending on the application, R_0 is chosen accordingly:

Objective	R_0 relative to R	Rationale
---	---	---
Maximize power transfer	$R_0 = R$	Balances internal and external power dissipation
Maximize efficiency	$R_0 \gg R$	Minimize internal losses, but reduces power delivered
Achieve specific voltage	$R_0 = (V_t / (V - V_t)) R$	For voltage regulation

Case Study: Practical Example

Suppose a battery has:

- emf $(V = 12\text{ V})$
- internal resistance $(R = 1\,\Omega)$

Question: To transfer maximum power, what external resistance R_0 should be connected?

Solution:

$$R_0 = R = 1\,\Omega$$

Power calculation at $R_0 = 1\,\Omega$:

$$I = \frac{V}{R + R_0} = \frac{12}{1 + 1} = 6\text{ A}$$
$$P_{\text{out}} = I^2 R_0 = 36 \times 1 = 36\text{ W}$$

Efficiency:

$$\eta = \frac{R_0}{R + R_0} = \frac{1}{2} = 50\%$$

This setup maximizes power transfer but results in significant internal energy loss.

Conclusion

The question "A Battery Has An emf of V and an Internal Resistance of R, What Resistance R, When Connected Across The" encapsulates a fundamental aspect of electrical circuit design and analysis. The classic solution, rooted

A Battery Has An Emf Of V And An Internal Resistance Of R What Resistance R When Connected Across The

A Battery Has An Emf Of V And An Internal Resistance Of R What Resistance R When Connected Across The

Related Articles

- [12\) A Horizontal Force Of 200 N Is Applied To Move A 55-kg Cart \(initially At Rest\) Across A 10 M Level](#)
- [What Does It Mean When Someone Says That People In The Western World And The Indians Of South American](#)
- [A Box Contains Ten Tickets, Labeled With The Numbers 11, 20, 20, 22, 23, 24, 29, 29, 30, 33. The Normal](#)

[Back to Home](#)