

The Capacitor Is Uncharged When The Switch Is Closed At $T=0$. Which Circuit Is Equivalent To This Circuit

The Capacitor Is Uncharged When The Switch Is Closed At $T=0$. Which Circuit Is Equivalent To This Circuit

Understanding the behavior of capacitors in electrical circuits is fundamental to analyzing and designing electronic systems. When a switch is closed at $T=0$ in a circuit containing a capacitor, the initial state of the capacitor significantly influences how the circuit responds over time. Specifically, the scenario where the capacitor is uncharged at the moment the switch is closed introduces unique characteristics and simplifies the analysis of the circuit's transient response. In this article, we will explore the implications of an initially uncharged capacitor at $T=0$, examine which circuit configurations are equivalent to this situation, and discuss the practical applications of these concepts in electrical engineering.

Understanding Capacitors in Circuits

Before delving into the specifics of the uncharged capacitor scenario, it is essential to review the fundamental properties of capacitors and their behavior in circuits.

Basic Properties of Capacitors

A capacitor is a passive electronic component that stores electrical energy in an electric field. Its key characteristics include:

- Capacitance (C): The measure of a capacitor's ability to store charge, expressed in farads (F).
- Voltage-Current Relationship: The current flowing through a capacitor is proportional to the rate of change of voltage across it:

$$i(t) = C \frac{dv(t)}{dt}$$

- Initial Conditions: The voltage across a capacitor at any instant depends on its prior charge. If uncharged, the voltage at $T=0$ is zero.

Charging and Discharging Behavior

- When connected to a voltage source, a capacitor charges up until the voltage across it matches the source voltage.
- During charging, the current initially is maximum and decreases exponentially.
- When discharging, the capacitor releases stored energy, and the voltage across it decreases accordingly.

The Significance of Initial Conditions in Transient Analysis

Initial conditions in circuits involving capacitors and inductors are crucial because they influence the transient response—the behavior of the circuit immediately after a change, such as closing a switch.

Initial Condition: Uncharged Capacitor at $T=0$

- The voltage across the capacitor at $T=0$ is zero:

$$v_C(0) = 0$$

- This simplifies the analysis, as the initial energy stored in the capacitor is zero.
- The circuit's response immediately after closing the switch can be modeled as if the capacitor is replaced by a short circuit (since initially, no voltage across it).

Why Is This Important?

- The initial uncharged state determines the initial current flow.
- It influences the shape of the transient response.
- It allows for the use of simplified equivalent circuits, facilitating easier analysis.

Analyzing the Circuit When the Switch Is Closed at $T=0$

Suppose we have a circuit with a voltage source, resistors, and a capacitor, with a switch that connects the source to the circuit at $T=0$.

Typical Circuit Configuration

- Before $T=0$: The switch is open; the capacitor is isolated and uncharged.
- At $T=0$: The switch is closed, connecting the circuit to the voltage source.

Initial Conditions and Circuit Behavior

- Since the capacitor is uncharged, the voltage across it at $T=0$ is zero.
- The initial current in the circuit is determined by the resistive elements and the source voltage, considering the capacitor as a short circuit at that instant.

Transient Response Analysis

The circuit's transient response can be modeled by:

- Writing the differential equations governing the circuit.
- Applying initial conditions (here, $v_C(0) = 0$).
- Solving for the voltage and current as functions of time.

Equivalent Circuits for the Uncharged Capacitor Scenario

When analyzing circuits with initially uncharged capacitors, certain simplified or equivalent circuits are used to facilitate understanding and calculations.

Series and Parallel Equivalent Circuits

- Series Equivalent: The capacitor behaves like a short circuit at $T=0$; thus, the initial circuit can be viewed as the original circuit with the capacitor replaced by a wire (short circuit).
- Parallel Equivalent: The initial voltage across the capacitor is zero, which corresponds to a zero-voltage source in parallel with the capacitor modeled as a short.

Step-by-Step Replacement Approach

1. At $T=0$, replace the capacitor with a short circuit because the voltage across it is zero.
2. Analyze the resulting resistor network to find the initial current and voltage.
3. Use these initial conditions to solve the circuit's differential equations for $T > 0$.

Practical Example: RC Circuit

Consider a simple RC circuit:

- Voltage source (V_s)
- Resistor (R)
- Capacitor (C)
- Switch that closes at $T=0$

Initial Conditions:

- $(v_C(0) = 0)$

Equivalent Circuit at $T=0$:

- The capacitor is replaced by a short circuit, so the initial current is:

$$i(0) = \frac{V_s}{R}$$

Mathematical Modeling and Solution

To analyze the circuit, differential equations are set up based on Kirchhoff's laws.

Formulating the Differential Equation

For an RC circuit:

$$V_s = R i(t) + v_C(t)$$

Since $v_C(t) = \frac{1}{C} \int i(t) dt$, differentiating yields:

$$\frac{d v_C(t)}{dt} = \frac{i(t)}{C}$$

Expressed as a first-order differential equation:

$$\frac{di(t)}{dt} + \frac{i(t)}{RC} = \frac{V_s}{R}$$

$$\frac{d v_C(t)}{dt} + \frac{1}{RC} v_C(t) = \frac{V_s}{RC}$$

\]

Initial condition:

\[

$$v_C(0) = 0$$

\]

Solution:

\[

$$v_C(t) = V_s \left(1 - e^{-\frac{t}{RC}}\right)$$

\]

Initial current:

\[

$$i(0) = \frac{V_s}{R}$$

\]

which aligns with the equivalent circuit where the capacitor acts as a short at $T=0$.

Practical Applications of Uncharged Capacitor Analysis

Understanding the equivalent circuits and initial conditions of uncharged capacitors is vital in various engineering applications.

Timing and Pulse Circuits

- RC circuits are used in timers; initial uncharged conditions are essential for predictable timing behavior.
- Charging curves determine the delay times for pulse generation.

Filter Design

- Capacitors are integral in filters; initial conditions influence transient responses affecting signal integrity.

Power Supply and Energy Storage

- Capacitors used for smoothing or energy storage rely on initial uncharged states for proper functioning during startup.

Transient Analysis in Electrical Systems

- Engineers use equivalent circuits to analyze faults, switching surges, and system dynamics efficiently.

Summary and Key Takeaways

- When a switch is closed at $T=0$ in a circuit with an uncharged capacitor, the initial voltage across the

capacitor is zero.

- The circuit can be modeled as if the capacitor is a short circuit at $T=0$, simplifying transient analysis.
- The initial current is determined by the resistive elements and the supply voltage, with the capacitor initially acting as a wire.
- The equivalent circuit at $T=0$ is crucial in solving differential equations governing the transient response.
- These concepts are fundamental in designing timing circuits, filters, and understanding power system transients.

Conclusion

Analyzing circuits with initially uncharged capacitors provides insights into transient behaviors that are vital in electrical engineering. Recognizing the equivalent circuit—where the capacitor behaves as a short at the moment of switching—allows engineers to simplify complex transient analyses and predict circuit responses accurately. Whether designing timers, filters, or power systems, understanding the initial conditions and their implications ensures reliable and efficient circuit performance.

Keywords: uncharged capacitor, transient response, equivalent circuit, RC circuit, initial conditions, circuit analysis, transient behavior, switching, electrical engineering

Frequently Asked Questions

What happens to the capacitor when the switch is closed at $T=0$ in an uncharged RC circuit?

At $T=0$, the uncharged capacitor acts like a short circuit, allowing current to flow abruptly, and then gradually charges over time.

Which circuit configuration is equivalent to an uncharged capacitor when the switch is just closed?

It is equivalent to a short circuit or a wire with negligible resistance at the instant the switch is closed, since the capacitor initially behaves like a short.

How does the initial current behave in a circuit with an uncharged capacitor at $T=0$?

The initial current is at its maximum because the uncharged capacitor presents zero voltage across its plates, acting like a short circuit.

What is the equivalent circuit immediately after closing the switch in an RC circuit with an uncharged capacitor?

The equivalent circuit is a simple resistor connected directly across the power supply, with the capacitor initially acting as a short circuit.

Why is the capacitor considered uncharged at $T=0$ when the switch is closed?

Because prior to closing the switch, no charge has accumulated on the capacitor plates, so its voltage is zero at $T=0$.

How does the equivalent circuit change over time after the switch is closed in an RC circuit?

Initially, the capacitor behaves like a short circuit, but as it charges, it gradually acts as an open circuit, changing the circuit's dynamics and voltage distribution.

Additional Resources

The Capacitor Is Uncharged When The Switch Is Closed At $T=0$. Which Circuit Is Equivalent To This Circuit?

Introduction

In the realm of electrical engineering and circuit analysis, understanding the behavior of capacitors during transient conditions is fundamental. When a switch in a circuit is closed at a specific time, particularly at $T=0$, the initial conditions of the capacitor significantly influence the circuit's subsequent response. A typical scenario involves a capacitor that is initially uncharged when the switch is closed at $T=0$. This situation raises an intriguing question: Which circuit is equivalent to this circuit under these initial conditions?

This article delves into this question, exploring the theoretical underpinnings, practical implications, and the equivalent circuit representations for circuits with an uncharged capacitor at $T=0$. Through detailed analysis, we aim to provide clarity for students, engineers, and researchers interested in transient circuit analysis.

Fundamental Concepts

Capacitors in Circuit Analysis

A capacitor is a two-terminal passive component that stores energy in the electric field between its plates. Its fundamental characteristic is its voltage-current relationship:

$$i(t) = C \frac{dv(t)}{dt}$$

where:

- $i(t)$ is the current flowing into the capacitor,
- $v(t)$ is the voltage across the capacitor,
- C is the capacitance.

Initial Conditions and Transient Response

The behavior of a circuit at the moment a switch is closed depends on the initial conditions of its energy-storing elements, primarily capacitors and inductors. Capacitors resist sudden changes in voltage, implying:

- Initial voltage across the capacitor (at $T=0^-$): $v(0^-)$.
- Voltage across the capacitor at $T=0^+$ (immediately after switching): $v(0^+)$.

If the capacitor is initially uncharged, then:

$$v(0^-) = 0$$

and consequently,

$$v(0^+) = 0.$$

This initial voltage condition is crucial because it determines how the circuit responds immediately after the switch closes.

The Scenario: Uncharged Capacitor at $T=0$

Description of the Circuit

Consider a generic circuit with a capacitor, some resistors, voltage sources, and a switch. When the switch opens or closes at $T=0$, the capacitor's state influences the overall transient response.

The key scenario under examination is:

- At $T=0$, the switch is closed.
- The capacitor is initially uncharged, i.e., $v(0^-) = 0$.

This setup is common in transient analysis problems, such as step responses in RC circuits, filter transient analyses, or energy storage studies.

Initial Conditions and Their Implications

Since the capacitor is initially uncharged, it acts as a short circuit at the very instant just after $T=0$ (assuming ideal conditions). This is because the voltage across an uncharged capacitor cannot change instantaneously, so:

$$v(0^+) = v(0^-) = 0$$

Consequently, the circuit's initial response is characterized by the capacitor behaving as a short circuit at $T=0^+$.

Equivalent Circuit Representation

Rationale for Equivalent Circuits

In transient circuit analysis, it's often useful to replace complex parts of the circuit with simpler, equivalent models that replicate the initial conditions and the circuit's behavior at specific moments.

For an uncharged capacitor at $T=0$, the equivalent circuit simplifies the capacitor to a specific element that models its instantaneous behavior, enabling easier analysis.

The Short-Circuit Model for an Uncharged Capacitor

The primary and most common approximation for an uncharged capacitor at the moment of switching is to model it as a short circuit at $T=0+$. This is because:

- The voltage across the capacitor cannot change instantaneously.
- Initially, the capacitor acts as a wire with zero voltage difference.

Thus, the equivalent circuit at $T=0+$ involves replacing the capacitor with a wire (short circuit), which simplifies the analysis of initial conditions.

Formal Equivalent Circuit

Given the above, the equivalent circuit for the original circuit at $T=0+$ when the capacitor is initially uncharged involves:

- Replacing the capacitor with a short circuit.
- Retaining all other circuit elements as they are.

This approach is valid for analyzing the initial current and voltage distributions immediately after the switch closure.

Analytical Approach to the Equivalent Circuit

Step-by-Step Analysis

1. Identify the initial conditions:

- $v_C(0^-) = 0$ (initially uncharged).
- $i_C(0^-) = 0$ (no initial current).

2. Replace the capacitor with a short circuit at $T=0^+$ to analyze initial behavior.

3. Solve the simplified circuit:

- Use standard circuit analysis techniques (node-voltage, mesh-current, superposition).

4. Determine the initial current and voltage:

- These initial values influence the subsequent transient response.

Mathematical Justification

The justification for replacing the capacitor with a short circuit at $T=0^+$ relies on the capacitor's voltage continuity:

$$v_C(0^+) = v_C(0^-) = 0.$$

Since the voltage cannot change instantaneously, at the moment of switching, the capacitor behaves as a zero impedance element, effectively a wire.

Practical Examples and Applications

Example 1: RC Step Response

Consider an RC circuit with a resistor (R) , a capacitor (C) , and a DC voltage source (V_s) :

- At $(t=0^-)$, the capacitor is uncharged.
- At $(t=0)$, the switch is closed, connecting the source.

Equivalent circuit at $T=0+$:

- The capacitor is replaced by a short circuit.
- The initial current through the resistor is:

$$i(0^+) = \frac{V_s}{R}.$$

This initial current sets the starting point for the exponential charging of the capacitor.

Example 2: Transient Behavior in Filter Circuits

In filter circuits, the initial conditions determine the transient response. When the capacitor is initially uncharged, modeling it as a short circuit simplifies the initial transient analysis, especially for calculating initial current flows and voltages.

Limitations and Considerations

While modeling an uncharged capacitor as a short circuit at $T=0+$ is a standard approach, certain caveats exist:

- Ideal Conditions: Assumes ideal components with no parasitic inductance or resistance.
- Instantaneous Behavior: Only valid for the initial moment immediately after switching.
- Subsequent Behavior: As time progresses, the capacitor's voltage increases, and the model no longer holds; the capacitor must be modeled as a voltage source with a specific voltage.

Broader Context: Which Circuit Is Equivalent?

The core question—which circuit is equivalent to this circuit when the capacitor is initially uncharged at $T=0$?—can be answered by:

- Replacing the capacitor with a short circuit at $T=0+$.
- Analyzing the resulting simpler circuit to determine initial currents and voltages.

This equivalent circuit allows engineers and students to comprehend the initial transient behavior without solving the entire complex circuit immediately.

Summary and Conclusions

The circuit is equivalent to the original circuit with the capacitor replaced by a short circuit at $T=0+$ when the capacitor is initially uncharged. This simplification captures the instantaneous response of the circuit immediately after the switch is closed.

Key takeaways:

- An uncharged capacitor acts as a short circuit at the instant of switching.
- The equivalent circuit for analyzing initial conditions is obtained by replacing the capacitor with a wire.
- This approach simplifies transient analysis and provides foundational insights into circuit behavior

during switching events.

Understanding this principle is essential for designing, analyzing, and troubleshooting circuits involving energy storage elements, especially during transient events. It underscores the importance of initial conditions in dynamic circuit analysis and highlights the utility of equivalent circuit models for simplifying complex analyses.

References

- Dorf, R. C., & Svoboda, J. A. (2010). Introduction to Electric Circuits. Wiley.
- Alexander, C. K., & Sadiku, M. N. O. (2012). Fundamentals of Electric Circuits. McGraw-Hill Education.
- Hayt, W. H., Kemmerly, J. E., & Durbin, S. M. (2018). Engineering Circuit Analysis. McGraw-Hill Education.

This comprehensive discussion provides a clear understanding of the equivalent circuit when a capacitor is initially uncharged at the moment a switch is closed, offering valuable insights for both theoretical study and practical application in electrical engineering.

The Capacitor Is Uncharged When The Switch Is Closed At $T = 0$ Which Circuit Is Equivalent To This Circuit

The Capacitor Is Uncharged When The Switch Is Closed At $T = 0$ Which Circuit Is Equivalent To This Circuit

Related Articles

- [The Deloitte Performance Review Process Is Based On Four Questions Called A\(n\) _____ And Is Conducted](#)

- [. Salts Are Formed By The Reaction Of An Acid And A Base. For Each Of The Following Combinations, Provide](#)
- [When Hurricanes Make Landfall, Damage Can Occur In A Number Of Ways. Choose The All Of The Ways In Which](#)

[Back to Home](#)