

A 1.50- F Capacitor Is Charging Through A 12.0- Resistor Using A 10.0- V Battery. What Will Be The Current

A 1.50- F Capacitor Is Charging Through A 12.0- Resistor Using A 10.0-V Battery. What Will Be The Current

Understanding how capacitors charge in electrical circuits is fundamental for students and professionals working in electronics and electrical engineering. In this article, we will explore the question: A 1.50-F capacitor is charging through a 12.0-Ω resistor using a 10.0-V battery. What will be the current during the charging process? We will delve into the principles of capacitor charging, apply relevant formulas, and examine how to compute the current at different moments. By the end, you'll have a clear understanding of the dynamics involved and how to analyze similar circuits.

Basics of Capacitor Charging in RC Circuits

Before diving into calculations, it's essential to understand the fundamental behavior of capacitors in resistor-capacitor (RC) circuits.

What Happens When a Capacitor Charges?

- When a voltage source (battery) is connected to a capacitor through a resistor, current initially flows into the capacitor, causing it to charge.
- As the capacitor accumulates charge, the voltage across its plates increases.
- The charging process continues until the voltage across the capacitor equals the battery voltage, at which point the current drops to zero.

Key Components in the Circuit

- Capacitor (C): Stores electrical energy; in our case, 1.50 farads.
- Resistor (R): Limits the current and controls the charging rate; here, 12.0 ohms.
- Voltage Source (V): Provides the potential difference to charge the capacitor; in this scenario, a 10.0-volt battery.

Understanding the Charging Equation of a

Capacitor

The voltage across a charging capacitor in an RC circuit over time is described by the exponential equation:

$$V_C(t) = V_{\text{source}} \times \left(1 - e^{-\frac{t}{RC}}\right)$$

where:

- $V_C(t)$ is the capacitor's voltage at time t ,
- V_{source} is the battery voltage (10.0 V),
- R is the resistance (12.0 Ω),
- C is the capacitance (1.50 F),
- t is the time since the start of charging,
- e is the base of the natural logarithm.

The current $I(t)$ at any moment during the charging process is given by:

$$I(t) = \frac{V_{\text{source}}}{R} \times e^{-\frac{t}{RC}}$$

This formula shows that the current decreases exponentially from its initial maximum value to zero as the capacitor charges.

Initial Current When Charging Starts

Let's analyze the initial current when the circuit is first connected at $t=0$.

Calculating the Initial Current

At $t=0$, the exponential term $(e^{-\frac{0}{RC}})$ equals 1, so:

$$I_{\text{initial}} = \frac{V_{\text{source}}}{R} \times 1 = \frac{10.0\text{ V}}{12.0\text{ }\Omega} \approx 0.833\text{ A}$$

Therefore, the initial current is approximately 0.833 amperes.

This is the maximum current in the circuit since the capacitor initially behaves like a short circuit (uncharged).

Current at Any Moment During Charging

The exponential nature of the charging process means the current diminishes over time. To find the current at a specific time (t) , use:

$$I(t) = I_{\text{initial}} \times e^{-\frac{t}{RC}}$$

where:

- (I_{initial}) is 0.833 A,
- (RC) is the time constant (τ) .

Calculating the Time Constant (τ)

The time constant (τ) indicates how quickly the capacitor charges:

$$\tau = R \times C = 12.0\,\Omega \times 1.50\,\text{F} = 18.0\,\text{s}$$

This means:

- After approximately 18 seconds, the current will have decayed to about 37% of its initial value.
- The voltage across the capacitor will be approaching 10 V but not yet fully there.

Example: Current After 18 Seconds

Calculate the current after one time constant:

$$I(18\,\text{s}) = 0.833\,\text{A} \times e^{-\frac{18\,\text{s}}{18\,\text{s}}} = 0.833\,\text{A} \times e^{-1} \\ \approx 0.833\,\text{A} \times 0.368 \approx 0.307\,\text{A}$$

At 18 seconds, the current drops to approximately 0.307 amperes.

Steady-State Current and Final Voltage

As time approaches infinity, the current approaches zero:

$$\lim_{t \rightarrow \infty} I(t) = 0\,\text{A}$$

Meanwhile, the capacitor's voltage approaches the battery voltage:

$$V_C(t) \rightarrow V_{\text{source}} = 10.0 \text{ V}$$

The charging process completes when the capacitor voltage equals 10 V, and the current ceases.

Practical Implications and Applications

Understanding the current during capacitor charging has vital applications:

- **Designing RC filters:** Knowing how quickly a capacitor charges helps in tuning filters for signals.
- **Timing circuits:** RC time constants determine delays in timer circuits.
- **Energy storage systems:** Calculating charging currents is crucial for safe and efficient energy storage.

Summary: Key Takeaways for Circuit Analysis

- The initial charging current for a 1.50 F capacitor through a 12.0 Ω resistor with a 10.0 V battery is approximately 0.833 A.
- The current decays exponentially with a time constant of 18 seconds.
- After one time constant, the current drops to about 0.307 A.
- The charging process continues until the capacitor voltage reaches the battery voltage, at which point the current is zero.

Conclusion

Analyzing the charging of a capacitor in an RC circuit involves understanding the exponential behavior of current and voltage over time. For the specific case of a 1.50-F capacitor charging through a 12.0- Ω resistor from a 10.0 V battery, the initial current is roughly 0.833 amperes, diminishing exponentially as the capacitor charges. Recognizing these principles allows engineers and students to design and analyze circuits effectively, ensuring optimal performance and safety.

Remember: Always consider the circuit parameters and use the appropriate formulas to determine current and voltage at any given moment during the

charging process.

Frequently Asked Questions

What is the initial current when the capacitor begins to charge in this circuit?

The initial current is given by Ohm's law: $I = V/R = 10.0 \text{ V} / 12.0 \text{ } \Omega = 0.833 \text{ A}$.

How does the current change as the capacitor charges over time?

The current decreases exponentially as the capacitor approaches its maximum charge, following $I(t) = (V/R) e^{(-t/RC)}$.

What is the time constant (τ) for this RC circuit?

The time constant $\tau = R \times C = 12.0 \text{ } \Omega \times 1.50 \text{ F} = 18.0 \text{ seconds}$.

How long does it take for the capacitor to reach approximately 63.2% of its maximum charge?

It takes one time constant, $\tau = 18.0 \text{ seconds}$, for the capacitor to reach about 63.2% of its maximum charge.

What is the maximum current in this circuit once the capacitor is fully charged?

Once fully charged, the current drops to zero because the capacitor acts like an open circuit.

Is the capacitor in this circuit a polar or non-polar capacitor, and does it matter in this context?

The problem doesn't specify, but typically, a capacitor with 1.50 F is likely a non-polar (e.g., electrolytic) capacitor; polarity matters for electrolytic types but not for the charging current calculation here.

What role does the resistor play during the charging process?

The resistor controls the rate of charging by limiting the current, affecting how quickly the capacitor reaches its maximum charge.

Can the current ever exceed the initial value during charging?

No, the current starts at its maximum (V/R) and decreases over time; it cannot exceed the initial current.

How would increasing the resistance affect the charging time and current?

Increasing the resistance would increase the time constant, slowing down the charging process and reducing the initial current.

Additional Resources

A 1.50-F Capacitor Is Charging Through A 12.0- Ω Resistor Using A 10.0-V Battery: What Will Be The Current?

In the realm of electrical engineering and physics, understanding the transient behavior of capacitors during charging processes is fundamental. The question of how current evolves as a capacitor charges through a resistor, especially with specific component values, is both theoretically intriguing and practically significant. This article explores the scenario where a 1.50-F capacitor charges through a 12.0- Ω resistor powered by a 10.0-V battery, focusing on determining the current at a specific moment and throughout the charging process.

Introduction to Capacitor Charging

Capacitors are passive electrical components capable of storing energy in an electric field. When connected to a voltage source through a resistor, the capacitor charges over time, with current initially at its maximum and gradually decreasing until the capacitor reaches the supply voltage. This process is governed by fundamental principles of circuit theory, particularly the exponential behavior characterized by the RC (resistance-capacitance) time constant.

Key concepts include:

- Initial current at the moment of connection
- Time-dependent current during the charging process
- Final steady-state current once fully charged

Understanding these aspects requires a deep dive into the governing equations and their implications for the specific component values at hand.

Fundamental Equations and Theory

Circuit Description

The basic circuit involves:

- A battery providing a constant voltage (V)
- A resistor (R) through which current flows
- A capacitor (C) that charges over time

The circuit diagram is straightforward: the battery, resistor, and capacitor are connected in series.

Governing Differential Equation

When the circuit is closed at $(t=0)$, the capacitor begins to charge. The voltage across the capacitor at time (t) , $(V_C(t))$, increases from zero to the battery voltage (V) . The current $(I(t))$ during charging is described by:

$$I(t) = \frac{V}{R} e^{-\frac{t}{RC}}$$

and the voltage across the capacitor evolves as:

$$V_C(t) = V \left(1 - e^{-\frac{t}{RC}}\right)$$

where:

- (V) = battery voltage
- (R) = resistance
- (C) = capacitance
- (t) = time elapsed since connection

Calculating the RC Time Constant

The RC time constant (τ) determines how quickly the capacitor charges:

$$\tau = R \times C$$

Substituting the given values:

$[$

$$R = 12.0\, \Omega$$

$$C = 1.50\, F$$

Results in:

$$\tau = 12.0\, \Omega \times 1.50\, F = 18.0\, \text{seconds}$$

This indicates that after approximately 18 seconds, the capacitor charges to about 63.2% of the supply voltage.

Determining the Initial Current

At $(t=0)$, the capacitor is uncharged, and the initial current (I_0) can be found directly from Ohm's Law:

$$I_0 = \frac{V}{R}$$

Substituting the known values:

$$I_0 = \frac{10.0\, V}{12.0\, \Omega} \approx 0.833\, \text{A}$$

Interpretation: The current starts at approximately 0.833 amperes immediately upon connection.

This initial current is maximal because the uncharged capacitor acts as a short circuit at $(t=0)$, allowing maximum current dictated solely by the resistor and battery voltage.

Current at a Specific Time

Suppose the question seeks the current at a particular time (t) . For example, after 10 seconds, the current is:

$$I(t) = I_0 e^{-\frac{t}{RC}}$$

Calculating:

$$I(10\text{ s}) = 0.833\text{ A} \times e^{-\frac{10}{18}} = 0.833\text{ A} \times e^{-0.555}$$

$$I(10\text{ s}) \approx 0.833\text{ A} \times 0.574 \approx 0.479\text{ A}$$

This illustrates the exponential decay of current during the charging process.

Final Steady-State Conditions

As $(t \rightarrow \infty)$, the exponential term approaches zero, and the current approaches zero:

$$I_{\text{final}} = 0\text{ A}$$

The capacitor becomes fully charged to the battery voltage, and the circuit reaches equilibrium where:

$$V_C = V = 10.0\text{ V}$$

At this point, no current flows through the resistor.

Practical Implications and Considerations

While the calculations provide clear theoretical insights, real-world scenarios may introduce complexities such as:

- Internal resistance of the battery
- Leakage currents in the capacitor
- Non-ideal behavior of components

However, for idealized calculations, the assumptions hold, offering a reliable basis for understanding the dynamic charging process.

Broader Context in Electrical Engineering

Understanding capacitor charging dynamics is critical for:

- Designing timing circuits (e.g., RC timers)
- Managing power supplies and filtering
- Developing energy storage systems

The specific values—particularly a large capacitance of 1.50 F—highlight applications where substantial energy storage or filtering is involved, such as in supercapacitors or specialized power electronics.

Summary and Conclusion

In summary, when a 1.50-F capacitor charges through a 12.0- Ω resistor powered by a 10.0-V battery, the initial current is approximately 0.833 A. This current decays exponentially with a time constant of 18 seconds, approaching zero as the capacitor becomes fully charged. The voltage across the capacitor asymptotically reaches the battery voltage, and the current at any instant can be precisely calculated using the exponential decay formula.

This analysis underscores the fundamental principles governing RC circuits and highlights the importance of understanding transient behaviors for effective circuit design and analysis.

Final Remarks

The scenario exemplifies core concepts in circuit theory and provides a practical framework for analyzing more complex systems. As technology advances, the ability to accurately model and predict capacitor charging behavior remains a cornerstone of electrical engineering, underpinning innovations across energy storage, signal processing, and electronic device design.

Keywords: capacitor charging, RC circuit, transient current, exponential decay, electrical engineering, energy storage, circuit analysis

[A 1 50 F Capacitor Is Charging Through A 12 0 Resistor Using A 10 0 V Battery What Will Be The Current](#)

A 1 50 F Capacitor Is Charging Through A 12 0 Resistor Using A 10 0 V Battery What Will Be The Current

Related Articles

- [Anne Recently Received A \\$1,000 Bonus At Work. She Has Decided To Invest The Extra Moneyin A Mutual Fund.](#)
- [For The Period July 1 To December 31, 2021, Prepare An Income Statement, Statement Of Stockholders Equity](#)
- [A Solid Is Formed By Adjoining Two Hemispheres To The Ends Of A Right Circular Cylinder. The Total Volume](#)

[Back to Home](#)