

# A 60-Hz 220-V-rms Source Supplies Power To A Load Consisting Of A Resistance In Series With An Inductance.

## A 60-Hz 220-V-rms Source Supplies Power To A Load Consisting Of A Resistance In Series With An Inductance.

Understanding the behavior of AC circuits is fundamental in electrical engineering, especially when dealing with real-world power systems. When a 60-Hz, 220-volt RMS AC source powers a load composed of a resistor in series with an inductor, the circuit exhibits unique characteristics governed by the principles of alternating current and impedance. This article comprehensively explores the analysis, power factors, and practical implications of such a series RL circuit, providing valuable insights for students, engineers, and professionals in the electrical domain.

---

## Fundamentals of Series RL Circuits

### What is a Series RL Circuit?

A series RL circuit consists of a resistor (R) and an inductor (L) connected in series across an AC voltage source. The primary features include:

- Resistive Component (R): Dissipates energy as heat and provides resistance to the flow of current.
- Inductive Component (L): Opposes changes in current due to its stored magnetic energy, causing phase shifts between voltage and current.
- Series Connection: Ensures the same current flows through both R and L, making the analysis straightforward.

### Impedance in a Series RL Circuit

In AC circuits, impedance (Z) generalizes resistance by considering reactive elements:

$$Z = R + jX_L$$

Where:

- (R): Resistance (ohms,  $\Omega$ )
- ( $X_L$ ): Inductive reactance (ohms,  $\Omega$ )
- (j): Imaginary unit

The inductive reactance  $(X_L)$  depends on frequency:

$$X_L = 2\pi f L$$

Given the source frequency  $(f = 60\text{ Hz})$ , the inductive reactance becomes:

$$X_L = 2\pi \times 60 \times L$$

The magnitude of impedance:

$$|Z| = \sqrt{R^2 + X_L^2}$$

The phase angle  $(\phi)$ :

$$\phi = \arctan\left(\frac{X_L}{R}\right)$$

This phase angle indicates that current lags the voltage by  $(\phi)$ .

---

## Analyzing Power in a 60-Hz 220-V RMS Series RL Circuit

### Source Voltage and Circuit Current

Given the source RMS voltage  $(V_{\text{rms}} = 220\text{ V})$  at 60 Hz, the current in the circuit is:

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{|Z|}$$

The phase difference between voltage and current causes the circuit to have a power factor less than 1.

### Power Calculation

The real power  $(P)$  consumed by the resistor:

$$P = V_{\text{rms}} \times I_{\text{rms}} \times \cos \phi$$

Where:

-  $(\cos \phi)$ : Power factor, representing the ratio of real power to apparent power.

The apparent power  $(S)$ :

$$S = V_{\text{rms}} \times I_{\text{rms}}$$

The reactive power ( $Q$ ):

$$Q = V_{\text{rms}} \times I_{\text{rms}} \times \sin \phi$$

Understanding these parameters aids in designing efficient electrical systems with minimal power loss.

---

## Impact of Resistance and Inductance on Circuit Behavior

### Effect of Resistance (R)

- Dissipates Power: Converts electrical energy into heat.
- Reduces Impedance: Lower  $R$  results in higher current for the same voltage.
- Improves Power Factor: Higher  $R$  tends to decrease phase angle ( $\phi$ ), closer to unity.

### Effect of Inductance (L)

- Introduces Reactive Power: Causes current to lag voltage.
- Increases Impedance: Larger  $L$  increases ( $X_L$ ), reducing current.
- Affects Power Factor: Higher inductance results in a lower power factor, which can lead to inefficient power usage.

---

## Calculating Power Parameters in a Series RL Circuit

### Step-by-Step Calculation

Suppose the resistance ( $R$ ) and inductance ( $L$ ) are known; for example:

- ( $R = 100\,\Omega$ )
- ( $L = 0.1\,\text{H}$ )

Calculate the following:

1. Inductive Reactance  $(X_L)$ :

$$X_L = 2\pi \times 60 \times 0.1 = 37.7\,\Omega$$

2. Impedance  $(Z)$ :

$$|Z| = \sqrt{100^2 + 37.7^2} \approx 107.4\,\Omega$$

3. Circuit Current  $(I_{rms})$ :

$$I_{rms} = \frac{220}{107.4} \approx 2.05\,A$$

4. Phase Angle  $(\phi)$ :

$$\phi = \arctan\left(\frac{37.7}{100}\right) \approx 20.7^\circ$$

5. Real Power  $(P)$ :

$$P = 220 \times 2.05 \times \cos 20.7^\circ \approx 220 \times 2.05 \times 0.936 \approx 423\,W$$

6. Reactive Power  $(Q)$ :

$$Q = 220 \times 2.05 \times \sin 20.7^\circ \approx 220 \times 2.05 \times 0.351 \approx 159\,VAR$$

These calculations demonstrate how resistance and inductance influence the power flow and efficiency.

---

## Practical Applications and Considerations

### Power Factor Correction

To optimize power usage, power factor correction methods are employed:

- Capacitors: Connected in parallel or series to offset inductive reactance.
- Power Factor Correction Devices: Used in industrial settings to reduce reactive power and improve efficiency.

### Effects on Power System Components

- Voltage Regulation: Inductive loads can cause voltage drops.
- Transformer Sizing: Larger impedance may necessitate larger transformers.
- Energy Losses: Increased reactive power leads to higher losses in transmission lines.

## Design Considerations

- Ensure the circuit components can handle the peak currents and voltages.
- Use power factor correction where necessary to reduce energy costs.
- Consider the impact of inductance on transient responses and circuit stability.

---

## Conclusion

A 60-Hz 220-V RMS source supplying a load consisting of a resistance in series with an inductance exhibits complex behavior characterized by impedance, phase shifts, and power factor considerations. Understanding the interplay between resistance and inductance allows engineers to optimize circuit performance, improve energy efficiency, and ensure the reliable operation of electrical systems. Proper analysis, including calculations of impedance, power, and reactive components, is essential for designing and managing AC circuits effectively.

Keywords: Series RL Circuit, Impedance, Power Factor, Inductive Reactance, AC Power Analysis, 60 Hz, 220 Volt RMS, Electrical Engineering, Power System Efficiency

## Frequently Asked Questions

### **What is the significance of a 60-Hz power supply for a load with resistance and inductance?**

A 60-Hz power supply provides a standard frequency in many regions, affecting the impedance and the phase angle between voltage and current in the R-L load, which influences power consumption and power factor.

### **How does the inductance in the series circuit affect the overall impedance and current flow?**

The inductance increases the total impedance of the circuit, causing the current to lag behind the voltage and reducing the overall current for a given voltage, compared to a purely resistive load.

### **What is the power factor in a series R-L circuit supplied by a 220 V RMS, 60 Hz source?**

The power factor is the cosine of the phase angle between voltage and current, which decreases with higher inductance. It can be calculated as  $\cos(\theta) = R / Z$ , where  $Z$  is the total impedance, indicating how efficiently the power is used.

## How can the power supplied to the load be calculated in this R-L circuit?

The real power can be calculated using  $P = V_{\text{rms}} I_{\text{rms}} \cos(\theta)$ , where  $V_{\text{rms}}$  is 220 V,  $I_{\text{rms}}$  is the current, and  $\cos(\theta)$  is the power factor. Alternatively,  $P = I_{\text{rms}}^2 R$ .

## What effect does increasing the inductance have on the circuit's power factor and energy consumption?

Increasing the inductance decreases the power factor (makes it more lagging), leading to less efficient power usage and potentially higher energy losses since more reactive power is present.

## How does the frequency of 60 Hz influence the inductive reactance in the circuit?

The inductive reactance ( $X_L$ ) is given by  $X_L = 2\pi fL$ , so at 60 Hz,  $X_L$  increases proportionally with the inductance  $L$ , affecting the impedance and the circuit's phase relationship.

## Additional Resources

A 60-Hz 220-V-rms Source Supplies Power To A Load Consisting Of A Resistance In Series With An Inductance

---

### Introduction

In the realm of electrical engineering, understanding how various sources supply power to different types of loads is fundamental. Among these, the scenario involving a 60-Hz, 220-V rms source feeding a series combination of resistance and inductance is a classic setup that encapsulates many core principles of AC circuit analysis. This configuration is prevalent in numerous practical applications, including power distribution, motor drives, and impedance matching networks.

This article aims to provide an in-depth investigation into the behavior of such a system, exploring the underlying theory, mathematical modeling, and practical implications. We will analyze how the source interacts with the load, examine the current and voltage relationships, and discuss the impact of the circuit parameters on power transfer efficiency. The investigation will delve into the concepts of impedance, power factor, and phase angle, culminating in a comprehensive understanding suitable for students, engineers, and researchers alike.

---

### Overview of the Power Supply and Load Configuration

#### The Power Source

The source in question operates at a frequency of 60 Hz, delivering an rms voltage of 220 V. This is a standard mains frequency in many regions worldwide, including North America and parts of Asia

and Africa. The source is assumed to be ideal, meaning it can supply the required current without internal impedance considerations unless specified otherwise.

Key parameters:

- Frequency,  $f = 60 \text{ Hz}$
- RMS Voltage,  $V_{\text{rms}} = 220 \text{ V}$

The Load

The load consists of a resistor  $R$  in series with an inductor  $L$ . This configuration is fundamental in AC circuit analysis because it introduces phase shifts and reactive power considerations that differ markedly from purely resistive loads.

Load components:

- Resistance,  $R$  (measured in ohms,  $\Omega$ )
- Inductance,  $L$  (measured in henrys, H)

The total impedance of the load,  $Z$ , governs current flow and power transfer characteristics.

---

Theoretical Foundations

Impedance in Series RL Circuits

In an AC circuit, impedance extends the concept of resistance to include reactive effects caused by inductance (and capacitance, if present). For a resistor  $R$  in series with an inductor  $L$ , the impedance  $Z$  is a complex quantity:

$$Z = R + jX_L$$

where:

- $X_L = 2\pi f L$  is the inductive reactance,
- $j$  is the imaginary unit ( $j^2 = -1$ ).

The magnitude of the impedance:

$$|Z| = \sqrt{R^2 + X_L^2}$$

The phase angle  $\phi$  between the source voltage and load current is given by:

$$\phi = \arctan \left( \frac{X_L}{R} \right)$$

which determines whether the load is leading or lagging the source voltage.

## Voltage and Current Relationships

Applying Ohm's law in the phasor domain:

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{|Z|} = \frac{220 \text{ V}}{\sqrt{R^2 + X_L^2}}$$

The load current is phase-shifted relative to the source voltage by  $\phi$ :

$$I_{\text{rms}} \text{ lags } V_{\text{rms}} \text{ by } \phi$$

---

## Power Analysis

### Real Power

The real (active) power delivered to the load:

$$P = V_{\text{rms}} I_{\text{rms}} \cos \phi$$

where  $\cos \phi$  is the power factor. It reflects the efficiency of power transfer from source to load.

### Reactive Power

Reactive power:

$$Q = V_{\text{rms}} I_{\text{rms}} \sin \phi$$

This power oscillates between the source and the inductor, not contributing to net energy consumption but affecting the circuit's reactive energy storage.

### Apparent Power

The apparent power:

$$S = V_{\text{rms}} I_{\text{rms}}$$

which combines real and reactive components, forming the apparent power vector in the complex

plane.

---

## Practical Implications of the Series RL Load

### Power Factor and Its Significance

A key concern in AC power systems is the power factor, defined as:

$$\text{Power factor} = \cos \phi$$

A low power factor indicates significant reactive power, leading to:

- Increased current for a given power level.
- Higher losses in transmission lines.
- The need for larger wiring and equipment ratings.

Improving the power factor involves adding capacitors or other reactive compensation methods.

### Voltage Drop Across Load Components

The voltage divides across  $R$  and  $X_L$ :

$$V_R = I_{\text{rms}} R$$
$$V_{X_L} = I_{\text{rms}} X_L$$

The total source voltage is the phasor sum of these components, with the phase shift  $\phi$  dictating their relative angles.

### Power Dissipation in the Resistance

Since the resistor dissipates real power as heat:

$$P_R = I_{\text{rms}}^2 R$$

The inductor, ideally, does not dissipate power but stores and releases energy.

---

## Analytical and Experimental Considerations

### Mathematical Modeling

Given specific load parameters, one can compute the impedance, phase angle, current, and power quantities:

1. Calculate  $X_L = 2\pi f L$ .
2. Determine  $|Z| = \sqrt{R^2 + X_L^2}$ .
3. Find the rms current  $I_{\text{rms}} = V_{\text{rms}} / |Z|$ .
4. Determine  $\phi = \arctan(X_L / R)$ .
5. Compute real, reactive, and apparent powers.

## Experimental Measurement

In real-world scenarios, measurements involve using:

- Voltmeters and ammeters capable of AC measurement.
- Power factor meters.
- Oscilloscopes for phase analysis.

Comparing theoretical calculations with measurements helps validate models and identify parasitic effects.

---

## Impacts of Circuit Parameters

### Effect of Resistance $(R)$

- Increasing  $(R)$  reduces the circuit's impedance magnitude.
- Leads to higher current at fixed voltage.
- Improves power factor if reactive effects are constant but increases power dissipation as heat.

### Effect of Inductance $(L)$

- Increasing  $(L)$  increases  $(X_L)$ , which:
  - Increases impedance magnitude.
  - Causes greater phase lag.
  - Decreases power factor, increasing reactive power.
- Can be tuned for desired circuit behavior, such as in filters or impedance matching.

## Frequency Variations

Although the source frequency is fixed at 60 Hz, understanding how  $(X_L)$  varies with frequency is crucial:

$$X_L = 2\pi f L$$

- Higher frequencies lead to larger reactance.
- This property is exploited in frequency-dependent applications like filters.

---

## Practical Applications and Considerations

### Power Distribution

Understanding the behavior of series RL loads is vital for designing efficient distribution systems, where reactive power compensation can improve overall system performance.

### Motor Loads

Many motors are inductive loads; modeling their power behavior using series RL circuits informs control strategies and efficiency improvements.

### Impedance Matching

Adjusting  $R$  and  $L$  allows engineers to optimize power transfer and minimize losses, especially in RF and telecommunications applications.

---

## Conclusion

The scenario where a 60-Hz 220-V-rms source supplies power to a load consisting of a resistance in series with an inductance encapsulates essential principles of AC circuit analysis. The interplay between resistance and inductance determines the impedance, phase relationships, and power transfer efficiency.

Understanding these relationships enables engineers to design, analyze, and optimize a wide array of electrical systems, from power distribution to electronic devices. Through theoretical models and practical measurements, the complex dynamics of such circuits can be thoroughly characterized, leading to improved performance and energy efficiency.

This detailed investigation underscores the importance of impedance understanding, power factor correction, and reactive power management in AC systems, forming a cornerstone of modern electrical engineering practice.

## **A 60 Hz 220 V Rms Source Supplies Power To A Load Consisting Of A Resistance In Series With An Inductance**

A 60 Hz 220 V Rms Source Supplies Power To A Load Consisting Of A Resistance In Series With An Inductance

## Related Articles

- [An Ounce Of Most Protein Foods Delivers About \\_\\_\\_\\_\\_ Of Protein.a. 10 Gramsb. 15 Gramsc. 1 Gramd. 7 Gramse.](#)

- [A Database Is Used Instead Of A Spreadsheet When \\_\\_\\_\\_\\_. Lists Of Data Involve A Single Theme Structures](#)
- [\(a\) Describe One Effect That Acid Deposition Has On Trees In A Forest Ecosystem. Scientists Are Interested](#)

[Back to Home](#)