

(3 POINTS) GIVEN A, B, AND C SKETCH A CIRCUIT FOR $F = ABC$ USING CMOS INVERTERS (DRAWN WITH JUST THE STANDARD

(3 POINTS) GIVEN A, B, AND C SKETCH A CIRCUIT FOR $F = ABC$ USING CMOS INVERTERS (DRAWN WITH JUST THE STANDARD

INTRODUCTION

IN DIGITAL LOGIC DESIGN, IMPLEMENTING BOOLEAN FUNCTIONS EFFICIENTLY USING CMOS TECHNOLOGY IS FUNDAMENTAL FOR CREATING LOW-POWER, HIGH-SPEED CIRCUITS. ONE COMMON TASK IS TO REALIZE A SPECIFIC LOGIC FUNCTION, SUCH AS $F = ABC$, WHERE A, B, AND C ARE INPUT VARIABLES. THIS ARTICLE PROVIDES AN IN-DEPTH GUIDE TO SKETCHING A CMOS CIRCUIT FOR THE FUNCTION $F = ABC$ USING ONLY STANDARD CMOS INVERTERS, WHICH ARE THE BASIC BUILDING BLOCKS IN CMOS LOGIC DESIGN. THE APPROACH INVOLVES UNDERSTANDING THE LOGIC FUNCTION, CONVERTING IT INTO A FORM SUITABLE FOR CMOS IMPLEMENTATION, AND THEN SYSTEMATICALLY DESIGNING THE CIRCUIT WITH INVERTERS AND THE NECESSARY LOGIC GATES.

UNDERSTANDING THE BOOLEAN FUNCTION $F = ABC$

NATURE OF THE FUNCTION

THE FUNCTION $F = ABC$ IS A THREE-INPUT AND FUNCTION, MEANING THE OUTPUT IS HIGH ONLY WHEN ALL THREE INPUTS A, B, AND C ARE HIGH. IT CAN BE EXPRESSED AS:

- $F = A \text{ AND } B \text{ AND } C$

THIS STRAIGHTFORWARD FORM LENDS ITSELF TO DIRECT IMPLEMENTATION USING CMOS LOGIC, BUT UNDERSTANDING THE UNDERLYING PRINCIPLES HELPS OPTIMIZE THE CIRCUIT.

BOOLEAN EXPRESSION ANALYSIS

- THE FUNCTION IS A PRODUCT (AND) OF THREE LITERALS.
- IT CAN BE DIRECTLY MAPPED TO A THREE-INPUT AND GATE, BUT IN CMOS LOGIC, AND FUNCTIONS ARE TYPICALLY IMPLEMENTED USING COMBINATIONS OF NANDS AND NORs, OR DIRECTLY VIA SERIES-CONNECTED TRANSISTORS.

IMPLEMENTING $F = ABC$ USING CMOS INVERTERS

BASIC CMOS COMPONENTS

- CMOS INVERTER: COMPRISES A PMOS TRANSISTOR AT THE TOP AND AN NMOS TRANSISTOR AT THE BOTTOM, FUNCTIONING AS A NOT GATE. IT INVERTS THE INPUT SIGNAL.
- CMOS LOGIC GATES: COMBINATIONS OF INVERTERS, NMOS, AND PMOS TRANSISTORS ARRANGED TO IMPLEMENT AND, OR, NAND, NOR, ETC.

STRATEGY FOR IMPLEMENTATION

SINCE THE TASK SPECIFIES USING ONLY CMOS INVERTERS (AND STANDARD CMOS LOGIC), THE KEY APPROACH IS:

- USE INVERTERS TO GENERATE COMPLEMENT SIGNALS OF INPUTS IF NEEDED.
- USE SERIES AND PARALLEL ARRANGEMENTS OF TRANSISTORS TO IMPLEMENT AND FUNCTIONALITY.
- RECOGNIZE THAT COMBINING INVERTERS WITH TRANSISTORS ALLOWS CONSTRUCTING ANY LOGIC GATE.

ALTERNATIVELY, THE FUNCTION CAN BE IMPLEMENTED USING DE MORGAN'S LAW:

- $F = ABC = \text{NOT} (\text{NOT } A + \text{NOT } B + \text{NOT } C)$

THIS SUGGESTS IMPLEMENTING A THREE-INPUT OR OF INVERTED INPUTS AND THEN INVERTING THE RESULT.

DESIGN APPROACH FOR $F = ABC$ USING CMOS INVERTERS

STEP 1: GENERATE INVERTED INPUTS

- USE CMOS INVERTERS TO PRODUCE A' , B' , AND C' (THE COMPLEMENTS OF A , B , AND C).
- THIS IS STRAIGHTFORWARD: EACH INVERTER TAKES A , B , OR C AS INPUT AND OUTPUTS A' , B' , C' .

STEP 2: IMPLEMENT OR OF A' , B' , AND C'

- THE OR FUNCTION OF A' , B' , AND C' CAN BE REALIZED BY COMBINING NMOS AND PMOS TRANSISTORS:
- IN CMOS, OR OPERATION CAN BE ACHIEVED BY CONNECTING THE INPUTS IN PARALLEL FOR THE PMOS NETWORK AND SERIES FOR THE NMOS NETWORK, OR VICE VERSA.
- FOR IMPLEMENTING $A' + B' + C'$, ARRANGE THE PMOS TRANSISTORS IN PARALLEL (SINCE PMOS CONDUCTS WHEN ITS GATE IS LOW), AND NMOS IN SERIES (SINCE NMOS CONDUCTS WHEN ITS GATE IS HIGH).

STEP 3: FINAL INVERSION TO GET F

- THE OUTPUT OF THE OR OF A' , B' , AND C' IS THEN INVERTED USING ANOTHER CMOS INVERTER TO PRODUCE F .

CONSTRUCTING THE CIRCUIT DIAGRAM

COMPONENTS NEEDED

- THREE CMOS INVERTERS FOR A , B , AND C .
- ADDITIONAL CMOS TRANSISTORS ARRANGED TO IMPLEMENT THE OR FUNCTION.
- A FINAL INVERTER TO INVERT THE OR OUTPUT, PRODUCING F .

STEP-BY-STEP CONSTRUCTION

1. INPUT INVERTERS:

- CONNECT A TO INVERTER 1, B TO INVERTER 2, C TO INVERTER 3.
- OUTPUTS: A' , B' , C' .

2. OR GATE FOR A' , B' , C' :

- CONNECT A' , B' , C' TO THE GATES OF PMOS TRANSISTORS ARRANGED IN PARALLEL AT THE TOP.
- CONNECT THE DRAIN OF EACH PMOS TO A COMMON NODE (SAY, NODE X).
- CONNECT THE SOURCES OF ALL PMOS TRANSISTORS TO V_{DD} (POWER SUPPLY).

- CONNECT THE DRAIN OF EACH NMOS TRANSISTOR IN SERIES, WITH GATES CONNECTED TO A' , B' , C' .
- THE SOURCE OF THE FIRST NMOS CONNECTED TO GROUND, AND THE SOURCE OF THE LAST NMOS CONNECTED TO NODE X.

3. FINAL INVERTER:

- CONNECT NODE X TO AN INVERTER.
- OUTPUT OF THIS INVERTER IS F , WHICH REALIZES THE ORIGINAL FUNCTION ABC .

COMPLETE CMOS CIRCUIT DIAGRAM OVERVIEW

- THE CIRCUIT STARTS WITH THREE INPUT INVERTERS GENERATING A' , B' , C' .
- THESE COMPLEMENTED SIGNALS FEED INTO A MULTI-TRANSISTOR NETWORK IMPLEMENTING THE OR FUNCTION.
- THE OR NETWORK'S OUTPUT IS INVERTED AGAIN TO PRODUCE F .
- THE ENTIRE DESIGN USES ONLY STANDARD CMOS INVERTERS AND THE ARRANGEMENT OF TRANSISTORS TO IMPLEMENT AND FUNCTIONALITY VIA DE MORGAN'S LAW.

ADVANTAGES OF THIS CMOS IMPLEMENTATION

- LOW POWER CONSUMPTION: CMOS LOGIC CONSUMES POWER ONLY DURING SWITCHING.
- HIGH NOISE MARGIN: CMOS CIRCUITS ARE ROBUST AGAINST NOISE.
- SCALABILITY: THE DESIGN CAN EASILY BE SCALED FOR MULTIPLE INPUTS OR INTEGRATED INTO LARGER SYSTEMS.

CONCLUSION

IMPLEMENTING THE BOOLEAN FUNCTION $F = ABC$ USING CMOS INVERTERS INVOLVES UNDERSTANDING THE LOGIC AND TRANSLATING IT INTO A COMBINATION OF INVERTERS AND TRANSISTOR ARRANGEMENTS. BY LEVERAGING DE MORGAN'S LAW, THE AND FUNCTION IS IMPLEMENTED THROUGH AN OR OF INVERTED INPUTS, WHICH IS WELL-SUITED TO CMOS TECHNOLOGY. THE STEP-BY-STEP PROCESS INCLUDES GENERATING INVERTED SIGNALS, CONSTRUCTING AN OR NETWORK WITH SERIES AND PARALLEL TRANSISTORS, AND FINAL INVERSION TO OBTAIN THE DESIRED OUTPUT. THIS APPROACH ILLUSTRATES THE POWER AND FLEXIBILITY OF CMOS TECHNOLOGY IN DIGITAL CIRCUIT DESIGN, EMPHASIZING THE IMPORTANCE OF SYSTEMATIC DESIGN STRATEGIES FOR EFFICIENT AND RELIABLE LOGIC IMPLEMENTATION.

FREQUENTLY ASKED QUESTIONS

HOW CAN YOU IMPLEMENT THE BOOLEAN FUNCTION $F = ABC$ USING CMOS INVERTERS?

TO IMPLEMENT $F = ABC$, CONNECT THREE AND GATES OR SERIES-CONNECTED NMOS TRANSISTORS FOR THE AND OPERATION, WITH THE COMPLEMENTARY CMOS LOGIC USING INVERTERS FOR EACH INPUT AND APPROPRIATE PULL-UP AND PULL-DOWN NETWORKS TO REALIZE THE AND OF A , B , AND C .

WHAT IS THE SIGNIFICANCE OF USING ONLY STANDARD CMOS INVERTERS IN DESIGNING THE CIRCUIT FOR $F = ABC$?

USING ONLY STANDARD CMOS INVERTERS SIMPLIFIES THE DESIGN, ENSURES LOW POWER CONSUMPTION, AND PROVIDES A RELIABLE, SCALABLE METHOD TO IMPLEMENT THE LOGIC FUNCTION WITH MINIMAL COMPLEXITY AND STANDARD COMPONENTS.

HOW DO YOU DRAW THE CMOS CIRCUIT FOR $F = ABC$ WITH JUST STANDARD INVERTERS?

START BY INVERTING INPUTS A , B , AND C USING THREE SEPARATE CMOS INVERTERS. THEN, CONNECT THE OUTPUTS OF THESE INVERTERS TO A SERIES OF NMOS TRANSISTORS (FOR AND OPERATION) AND PARALLEL PMOS TRANSISTORS (FOR PULL-UP)

TO REALIZE THE AND FUNCTION, ENSURING ONLY THE CORRECT LOGIC LEVELS ARE OUTPUT BASED ON ALL INPUTS BEING HIGH.

WHY IS IT IMPORTANT TO UNDERSTAND THE CMOS IMPLEMENTATION OF SIMPLE FUNCTIONS LIKE $F = ABC$?

UNDERSTANDING CMOS IMPLEMENTATION OF FUNCTIONS LIKE $F = ABC$ HELPS IN DESIGNING EFFICIENT DIGITAL CIRCUITS, OPTIMIZING POWER CONSUMPTION, AND ENSURING CORRECT LOGIC BEHAVIOR USING STANDARD CMOS COMPONENTS, WHICH IS FUNDAMENTAL IN VLSI DESIGN.

WHAT ARE THE KEY STEPS TO SKETCH A CMOS CIRCUIT FOR $F = ABC$ USING ONLY STANDARD INVERTERS?

THE KEY STEPS INCLUDE: (1) INVERT EACH INPUT A, B, AND C USING STANDARD CMOS INVERTERS, (2) CONNECT THESE INVERTED SIGNALS THROUGH SERIES NMOS TRANSISTORS TO FORM THE AND LOGIC, AND (3) CONNECT THE OUTPUTS VIA PARALLEL PMOS TRANSISTORS TO ACHIEVE THE CORRECT LOGIC LEVEL OUTPUT FOR F.

CAN YOU EXPLAIN HOW THE CMOS INVERTERS AND TRANSISTORS WORK TOGETHER TO IMPLEMENT THE AND FUNCTION FOR $F = ABC$?

YES, THE CMOS INVERTERS INVERT THE INPUTS A, B, AND C. THE SERIES CONNECTION OF NMOS TRANSISTORS CONDUCTS ONLY WHEN ALL INPUTS ARE HIGH (ORIGINAL INPUTS ARE HIGH), PRODUCING A LOW OUTPUT IN THE PULL-DOWN NETWORK. CONVERSELY, THE PARALLEL PMOS TRANSISTORS PULL THE OUTPUT HIGH WHEN ANY INPUT IS LOW, THUS REALIZING THE AND FUNCTION WITH COMPLEMENTARY CMOS LOGIC.

ADDITIONAL RESOURCES

COMPREHENSIVE ANALYSIS AND CIRCUIT DESIGN FOR $F = ABC$ USING CMOS INVERTERS

INTRODUCTION TO CMOS LOGIC DESIGN AND THE FUNCTION $F = ABC$

IN THE REALM OF DIGITAL LOGIC DESIGN, CMOS (COMPLEMENTARY METAL-OXIDE-SEMICONDUCTOR) TECHNOLOGY STANDS AS A DOMINANT APPROACH DUE TO ITS LOW POWER CONSUMPTION, HIGH NOISE IMMUNITY, AND SCALABILITY. WHEN DESIGNING COMBINATIONAL LOGIC FUNCTIONS, CMOS LOGIC OFFERS A SYSTEMATIC METHODOLOGY BY COMBINING P-TYPE AND N-TYPE MOSFETS TO IMPLEMENT ANY BOOLEAN FUNCTION EFFICIENTLY.

THE BOOLEAN FUNCTION $F = ABC$ IS A THREE-VARIABLE AND OPERATION, WHICH OUTPUTS HIGH (LOGIC 1) ONLY WHEN ALL THREE INPUTS A, B, AND C ARE HIGH. ITS IMPLEMENTATION VIA CMOS LOGIC INVOLVES UNDERSTANDING THE INTRINSIC CHARACTERISTICS OF CMOS INVERTERS AND THE SYSTEMATIC ARRANGEMENT OF TRANSISTORS TO REALIZE THE AND FUNCTION.

THIS DISCUSSION AIMS TO PROVIDE A DETAILED, STEP-BY-STEP GUIDE TO SKETCHING THE CIRCUIT FOR $F = ABC$ USING ONLY STANDARD CMOS INVERTERS—THAT IS, USING THE BASIC CMOS INVERTER STRUCTURE WITHOUT ADDITIONAL COMPLEX LOGIC GATES. WE WILL EXPLORE THE LOGIC DESIGN PRINCIPLES, THE STEP-BY-STEP SYNTHESIS OF THE CIRCUIT, AND THE PRACTICAL CONSIDERATIONS INVOLVED IN SUCH AN IMPLEMENTATION.

UNDERSTANDING THE BOOLEAN FUNCTION AND ITS IMPLEMENTATION STRATEGY

BOOLEAN EXPRESSION AND TRUTH TABLE

THE FUNCTION $F = ABC$ IS A SIMPLE THREE-INPUT AND FUNCTION:

A	B	C	F = ABC
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

THE OUTPUT IS HIGH ONLY WHEN ALL INPUTS ARE HIGH, WHICH CHARACTERIZES A STRAIGHTFORWARD AND OPERATION.

LOGIC DESIGN APPROACH USING CMOS

DESIGNING $F = ABC$ WITH CMOS LOGIC INVOLVES TRANSLATING THE BOOLEAN FUNCTION INTO A NETWORK OF PMOS AND NMOS TRANSISTORS THAT IMPLEMENT THE AND FUNCTION:

- IN CMOS LOGIC, THE PULL-UP NETWORK (PUN) IS CONSTRUCTED USING PMOS TRANSISTORS, WHICH PULL THE OUTPUT HIGH WHEN THE FUNCTION'S INPUTS SATISFY CERTAIN CONDITIONS.
- THE PULL-DOWN NETWORK (PDN) EMPLOYS NMOS TRANSISTORS, WHICH PULL THE OUTPUT LOW UNDER SPECIFIC INPUT CONDITIONS.

THE KEY PRINCIPLE IS:

- FOR AND FUNCTIONS, THE PMOS NETWORK IS DESIGNED AS A PARALLEL COMBINATION OF PMOS TRANSISTORS (SINCE PMOS TRANSISTORS CONDUCT WHEN THEIR GATE VOLTAGE IS LOW, I.E., 0), AND
- THE NMOS NETWORK IS ARRANGED AS A SERIES OF NMOS TRANSISTORS (SINCE NMOS TRANSISTORS CONDUCT WHEN THEIR GATE VOLTAGE IS HIGH, I.E., 1).

THUS, FOR $F = ABC$, THE STANDARD CMOS IMPLEMENTATION INVOLVES:

- SERIES CONNECTION OF NMOS TRANSISTORS FOR A, B, AND C IN THE PULL-DOWN NETWORK.
- PARALLEL CONNECTION OF PMOS TRANSISTORS FOR A, B, AND C IN THE PULL-UP NETWORK.

THIS CONFIGURATION ENSURES THAT THE CIRCUIT OUTPUTS A HIGH ONLY WHEN ALL INPUTS ARE HIGH, MATCHING THE AND FUNCTION.

DESIGNING THE CMOS CIRCUIT USING STANDARD INVERTERS

BASIC CONCEPT OF CMOS INVERTERS

BEFORE DELVING INTO THE COMBINED CIRCUIT, IT IS CRUCIAL TO UNDERSTAND THE FUNDAMENTAL CMOS INVERTER:

- CONSISTS OF A PMOS TRANSISTOR CONNECTED FROM V_{DD} (POSITIVE SUPPLY VOLTAGE) TO THE OUTPUT, AND AN NMOS TRANSISTOR CONNECTED FROM THE OUTPUT TO GROUND.
- INPUT IS CONNECTED TO THE GATES OF BOTH TRANSISTORS.
- WHEN THE INPUT IS LOW (0), PMOS CONDUCTS, CONNECTING THE OUTPUT TO V_{DD} , RESULTING IN A HIGH OUTPUT.
- WHEN THE INPUT IS HIGH (1), NMOS CONDUCTS, CONNECTING THE OUTPUT TO GROUND, RESULTING IN A LOW OUTPUT.

THIS BASIC INVERTER IS THE BUILDING BLOCK FOR MORE COMPLEX LOGIC CIRCUITS.

METHODOLOGY FOR USING INVERTERS TO BUILD AND FUNCTION

IMPLEMENTING MULTI-INPUT AND FUNCTIONS USING ONLY INVERTERS IS NOT STRAIGHTFORWARD BECAUSE INVERTERS ALONE CANNOT PERFORM AND OR FUNCTIONS DIRECTLY. USUALLY, THE PROCESS INVOLVES:

- CREATING THE NECESSARY LOGIC FUNCTIONS BY COMBINING INVERTERS, IN SOME CASES, WITH TRANSISTOR ARRANGEMENTS (SERIES/PARALLEL).
- USING INVERTERS TO GENERATE COMPLEMENTED SIGNALS (E.G., A AND A' , B AND B' , ETC.).
- CONSTRUCTING THE DESIRED LOGIC BY APPROPRIATELY CONNECTING INVERTERS AND TRANSISTOR NETWORKS.

HOWEVER, SINCE THE TASK EMPHASIZES USING STANDARD CMOS INVERTERS (DRAWN WITH JUST THE BASIC INVERTER STRUCTURE), THE TYPICAL APPROACH INVOLVES:

- GENERATING THE COMPLEMENTED SIGNALS OF A , B , AND C THROUGH INVERTERS.
- COMBINING THESE SIGNALS IN TRANSISTOR NETWORKS CONFIGURED AS PER CMOS LOGIC DESIGN PRINCIPLES.

IN THE CONTEXT OF THE FUNCTION $F = ABC$, THE PRIMARY APPROACH INVOLVES:

- USING INVERTERS TO GENERATE A' , B' , AND C' (COMPLEMENTED SIGNALS).
- IMPLEMENTING THE AND OPERATION BY COMBINING THESE SIGNALS IN A NETWORK OF TRANSISTORS ARRANGED IN SERIES AND PARALLEL CONFIGURATIONS.

STEP-BY-STEP CMOS CIRCUIT DESIGN FOR $F = ABC$

STEP 1: GENERATE COMPLEMENTED INPUTS

- INVERTER FOR A : CONNECT INPUT A TO THE GATE OF AN INVERTER. THE INVERTER OUTPUTS A' .
- INVERTER FOR B : CONNECT INPUT B TO THE GATE OF ANOTHER INVERTER. THE INVERTER OUTPUTS B' .
- INVERTER FOR C : CONNECT INPUT C TO THE GATE OF A THIRD INVERTER. THE INVERTER OUTPUTS C' .

THESE COMPLEMENTED SIGNALS ARE ESSENTIAL IF IMPLEMENTING CERTAIN LOGIC FUNCTIONS, ESPECIALLY WHEN REALIZING COMPLEX LOGIC FUNCTIONS WITH MINIMAL TRANSISTOR COUNTS.

STEP 2: CONSTRUCTING THE PULL-DOWN NETWORK (SERIES OF NMOS TRANSISTORS)

FOR THE AND FUNCTION, THE PULL-DOWN NETWORK (WHICH PULLS THE OUTPUT TO GROUND WHEN THE FUNCTION IS FALSE) IS DESIGNED AS:

- SERIES CONNECTION OF THREE NMOS TRANSISTORS CONTROLLED BY INPUTS A, B, AND C.

CONFIGURATION:

- NMOS TRANSISTOR 1: GATE CONNECTED TO A
- NMOS TRANSISTOR 2: GATE CONNECTED TO B
- NMOS TRANSISTOR 3: GATE CONNECTED TO C
- SOURCE OF TRANSISTOR 1 CONNECTED TO THE SOURCE OF TRANSISTOR 2, AND SO ON, FORMING A SERIES CHAIN.
- DRAIN OF TRANSISTOR 3 CONNECTED TO THE OUTPUT NODE.

OPERATION:

- ALL THREE TRANSISTORS CONDUCT SIMULTANEOUSLY ONLY WHEN A, B, AND C ARE HIGH (ALL GATES AT LOGIC 1).
- THIS PULLS THE OUTPUT TO GROUND, RESULTING IN $F = 0$ IN ALL OTHER CASES.

STEP 3: CONSTRUCTING THE PULL-UP NETWORK (PARALLEL OF PMOS TRANSISTORS)

THE PULL-UP NETWORK (WHICH PULLS THE OUTPUT HIGH WHEN THE FUNCTION IS TRUE) IS CONSTRUCTED AS:

- PARALLEL CONNECTION OF THREE PMOS TRANSISTORS CONTROLLED BY A, B, AND C.

CONFIGURATION:

- PMOS TRANSISTOR 1: GATE CONNECTED TO A
- PMOS TRANSISTOR 2: GATE CONNECTED TO B
- PMOS TRANSISTOR 3: GATE CONNECTED TO C
- ALL THEIR SOURCES CONNECTED TO V_{DD}
- THEIR DRAINS CONNECTED TOGETHER AT THE OUTPUT NODE

OPERATION:

- ANY ONE OF A, B, OR C BEING LOW (0) TURNS OFF THE CORRESPONDING PMOS TRANSISTOR.
- ONLY WHEN ALL THREE ARE HIGH (1) DO ALL PMOS TRANSISTORS CONDUCT, CONNECTING THE OUTPUT TO V_{DD} , PRODUCING $F = 1$.

COMPLETE CMOS CIRCUIT SKETCH WITH STANDARD INVERTERS

NOW, INTEGRATING THE ABOVE LOGIC INTO A COMPLETE CIRCUIT:

1. INPUT SIGNALS A, B, C ARE FED DIRECTLY INTO THE TRANSISTOR GATES OF THE PULL-DOWN NETWORK (NMOS TRANSISTORS IN SERIES).
2. THE SAME INPUTS ARE CONNECTED DIRECTLY TO THE GATES OF THE PMOS TRANSISTORS IN THE PULL-UP NETWORK (PARALLEL CONFIGURATION).

3. INVERTERS ARE USED TO GENERATE COMPLEMENTED SIGNALS A' , B' , C' AS NEEDED FOR IMPLEMENTING MORE COMPLEX FUNCTIONS OR OPTIMIZING TRANSISTOR ARRANGEMENTS.

4. THE OUTPUT NODE IS CONNECTED TO:

- THE DRAIN OF THE LAST NMOS TRANSISTOR IN SERIES (PULL-DOWN NETWORK).
- THE DRAIN OF THE LAST PMOS TRANSISTOR IN PARALLEL (PULL-UP NETWORK).

5. THE POWER SUPPLY V_{DD} CONNECTS TO THE SOURCES OF ALL PMOS TRANSISTORS.

6. THE GROUND CONNECTS TO THE SOURCES OF ALL NMOS TRANSISTORS.

NOTE: SINCE THE FUNCTION $F = ABC$ IS A STRAIGHTFORWARD AND, THE CIRCUIT CAN BE DIRECTLY REALIZED USING THE SERIES AND PARALLEL TRANSISTOR ARRANGEMENTS WITHOUT ADDITIONAL INVERTERS. THE INVERTERS PRIMARILY SERVE TO GENERATE COMPLEMENTARY SIGNALS IF NEEDED FOR FURTHER LOGIC.

PRACTICAL CONSIDERATIONS AND OPTIMIZATION

MINIMIZING TRANSISTOR COUNT

- FOR THE SIMPLE AND FUNCTION, THE MINIMAL CMOS IMPLEMENTATION INVOLVES 3 PMOS TRANSISTORS IN PARALLEL AND 3 NMOS TRANSISTORS IN SERIES.
- ADDITIONAL INVERTERS ARE UNNECESSARY UNLESS THE LOGIC REQUIRES COMPLEMENTED SIGNALS.

POWER CONSUMPTION AND SPEED

- CMOS LOGIC IS POWER-EFFICIENT BECAUSE CURRENT FLOWS ONLY DURING SWITCHING.
- THE SERIES AND PARALLEL ARRANGEMENTS INFLUENCE THE SWITCHING SPEED; SERIES NMOS TRANSISTORS INCREASE DELAY, SO CAREFUL LAYOUT AND SIZING ARE CRUCIAL.

PHYSICAL LAYOUT AND PARASITICS

3 POINTS GIVEN A B AND C SKETCH A CIRCUIT FOR $F = ABC$ USING CMOS INVERTERS
DRAWN WITH JUST THE STANDARD

3 POINTS GIVEN A B AND C SKETCH A CIRCUIT FOR $F = ABC$ USING CMOS INVERTERS
DRAWN WITH JUST THE STANDARD

RELATED ARTICLES

- [HECTOR BELIEVES THAT A LAW UNDER WHICH HE WAS CONVICTED FOR A](#)

CRIME VIOLATES THE CONSTITUTION. IF ULTIMATELY

- A FIVE-QUESTION MULTIPLE-CHOICE QUIZ HAS FIVE CHOICES FOR EACH ANSWER.
USE THE RANDOM NUMBER TABLE PROVIDED,
- PAPER CORP. PURCHASED 70% OF THE OUTSTANDING SHARES OF SAND LTD.
ON JANUARY 1, YEAR 2, AT A COST OF \$87,850.

[BACK TO HOME](#)